

Summary

A summary of the rules for finding the A circuit and β for a given series-shunt feedback amplifier of the form in Fig. 8.10(a) is given in Fig. 8.11. As for using the feedback formulas in Eqs. (8.10) and (8.12) to determine the input and output resistances, it is important to note that:

1. R_i and R_o are the input and output resistances, respectively, of the A circuit in Fig. 8.11(a).
2. R_{if} and R_{of} are the input and output resistances, respectively, of the feedback amplifier, including R_s and R_L [see Fig. 8.10(a)].
3. The actual input and output resistances of the feedback amplifier usually exclude R_s and R_L . These are denoted R_{in} and R_{out} in Fig. 8.10(a) and can be easily determined as

$$R_{in} = R_{if} - R_s$$

$$R_{out} = 1 / \left(\frac{1}{R_{of}} - \frac{1}{R_L} \right)$$

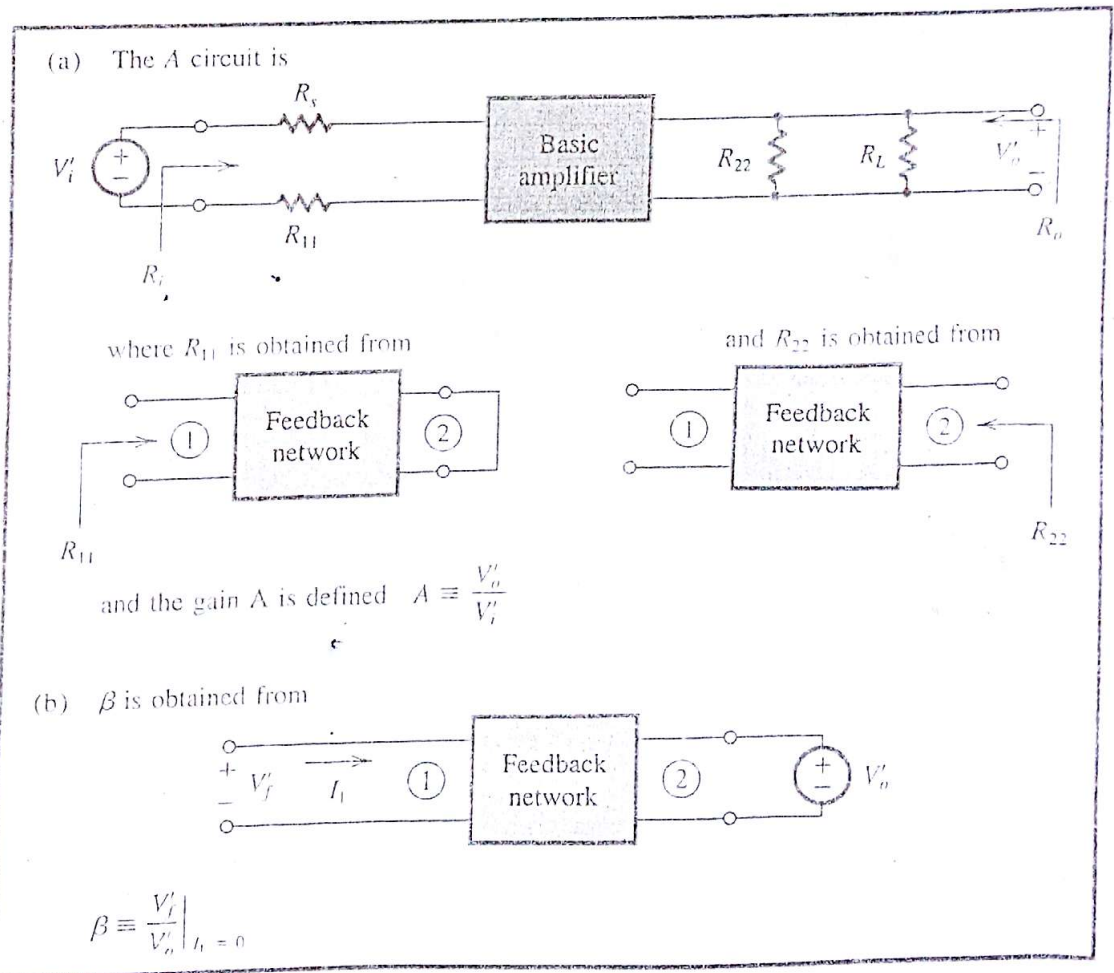


Fig. 8.11 Summary of the rules for finding the A circuit and β for the voltage-sampling series-mixing case of Fig. 8.10(a).

Voltage Amplifier

Gain

Rif
Routf

2

EXAMPLE 8.1

Figure 8.12(a) shows an op amp connected in the noninverting configuration. The op amp has an open-loop gain μ , a differential input resistance R_{id} , and an output resistance r_o . Recall that in our analysis of op-amp circuits in Chapter 2, we neglected the effects of R_{id} (assumed it to be infinite) and of r_o (assumed it to be zero). Here we wish to use the feedback method to analyze the circuit taking both R_{id} and r_o into account. Find expressions for A , β , the closed-loop gain V_o/V_s , the input resistance R_{in} (see Fig. 8.12a), and the output resistance R_{out} . Also find numerical values, given $\mu = 10^4$, $R_{id} = 100 \text{ k}\Omega$, $r_o = 1 \text{ k}\Omega$, $R_L = 2 \text{ k}\Omega$, $R_1 = 1 \text{ k}\Omega$, $R_2 = 1 \text{ M}\Omega$, and $R_s = 10 \text{ k}\Omega$.

SOLUTION

We observe that the feedback network consists of R_2 and R_1 . This network samples the output voltage V_o and provides a voltage signal (across R_1) that is mixed in series with the input source V_s .

The A circuit can be easily obtained following the rules of Fig. 8.11, and is shown in Fig. 8.12(b). For this circuit we can write by inspection

$$A \equiv \frac{V_o'}{V_i'} = \mu \frac{[R_L // (R_1 + R_2)]}{[R_L // (R_1 + R_2)] + r_o} \frac{R_{id}}{R_{id} + R_s + (R_1 // R_2)}$$

For the values given, we find that $A \approx 6000 \text{ V/V}$.

The circuit for obtaining β is shown in Fig. 8.12(c), from which we obtain

$$\beta \equiv \frac{V_f'}{V_o'} = \frac{R_1}{R_1 + R_2} \approx 10^{-3} \text{ V/V}$$

The voltage gain with feedback is now obtained as

$$A_f \equiv \frac{V_o}{V_s} = \frac{A}{1 + A\beta} = \frac{6000}{7} = 857 \text{ V/V}$$

The input resistance R_{if} determined by the feedback equations is the resistance seen by the external source (see Fig. 8.12a), and is given by

$$R_{if} = R_i(1 + A\beta)$$

where R_i is the input resistance of the A circuit in Fig. 8.12(b):

$$R_i = R_s + R_{id} + (R_1 // R_2)$$

For the values given, $R_i \approx 111 \text{ k}\Omega$, resulting in


$$R_{if} = 111 \times 7 = 777 \text{ k}\Omega$$

This, however, is not the resistance asked for. What is required is R_{in} , indicated in Fig. 8.12(a). To obtain R_{in} we subtract R_s from R_{if} :


$$R_{in} = R_{if} - R_s$$

For the values given, $R_{in} = 739 \text{ k}\Omega$. The resistance R_{of} given by the feedback equations is


3

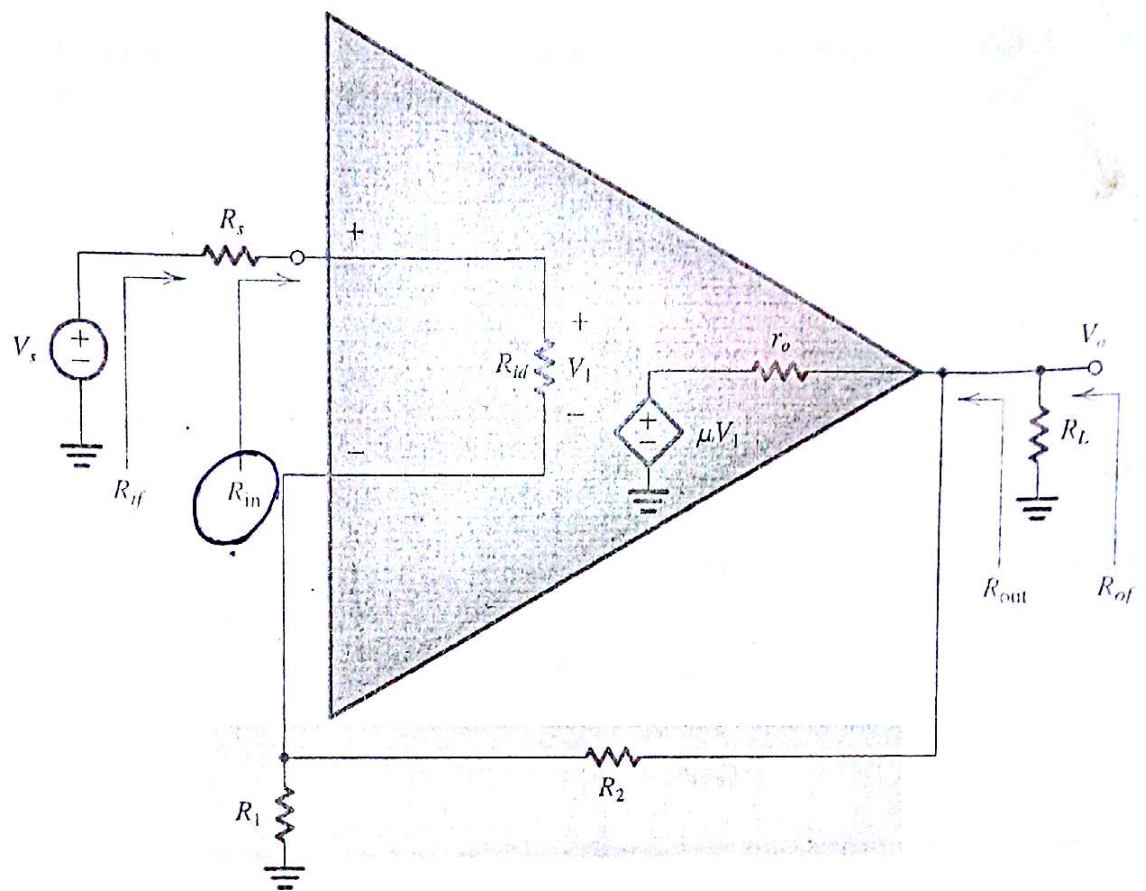

(a)

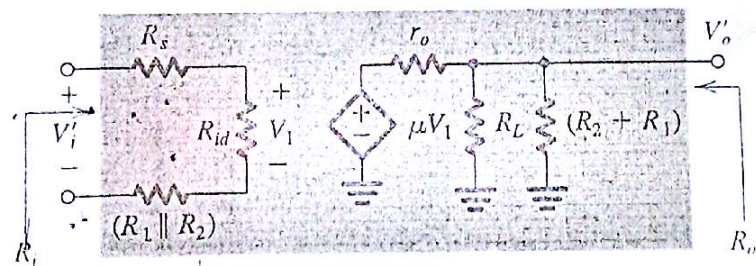

(b)

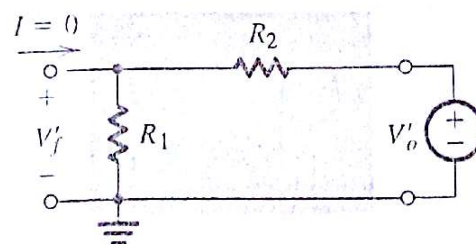

(c)

Fig. 8.12 Circuits for Example 8.1.

the output resistance of the feedback amplifier, including the load resistance R_L , as indicated in Fig. 8.12(a). R_{of} is given by

$$R_{of} = \frac{R_o}{1 + A\beta}$$

where R_o is the output resistance of the A circuit. R_o can be obtained by inspection of Fig. 8.12(b) as

$$R_o = r_o // R_L // (R_2 + R_1)$$

For the values given, $R_o \approx 667 \Omega$, and

$$R_{of} = \frac{667}{7} = 95.3 \Omega$$

The resistance asked for, R_{out} , is the output resistance of the feedback amplifier excluding R_L . From Fig. 8.12(a) we see that

$$R_{of} = R_{out} // R_L$$

Thus

$$R_{out} \approx 100 \Omega$$

Exercises

8.4 If the op amp of Example 8.1 has a uniform -6 -dB/octave high-frequency rolloff with $f_{3dB} = 1$ kHz, find the 3-dB frequency of the closed-loop gain V_o/V_s .

Ans. 7 kHz

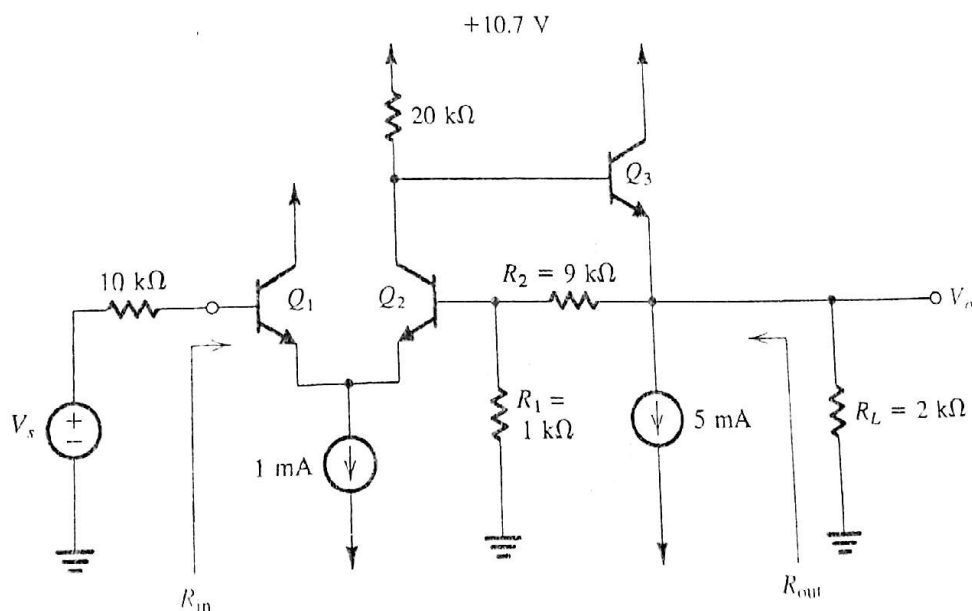


Fig. E8.5

Transconductance
Amplifier

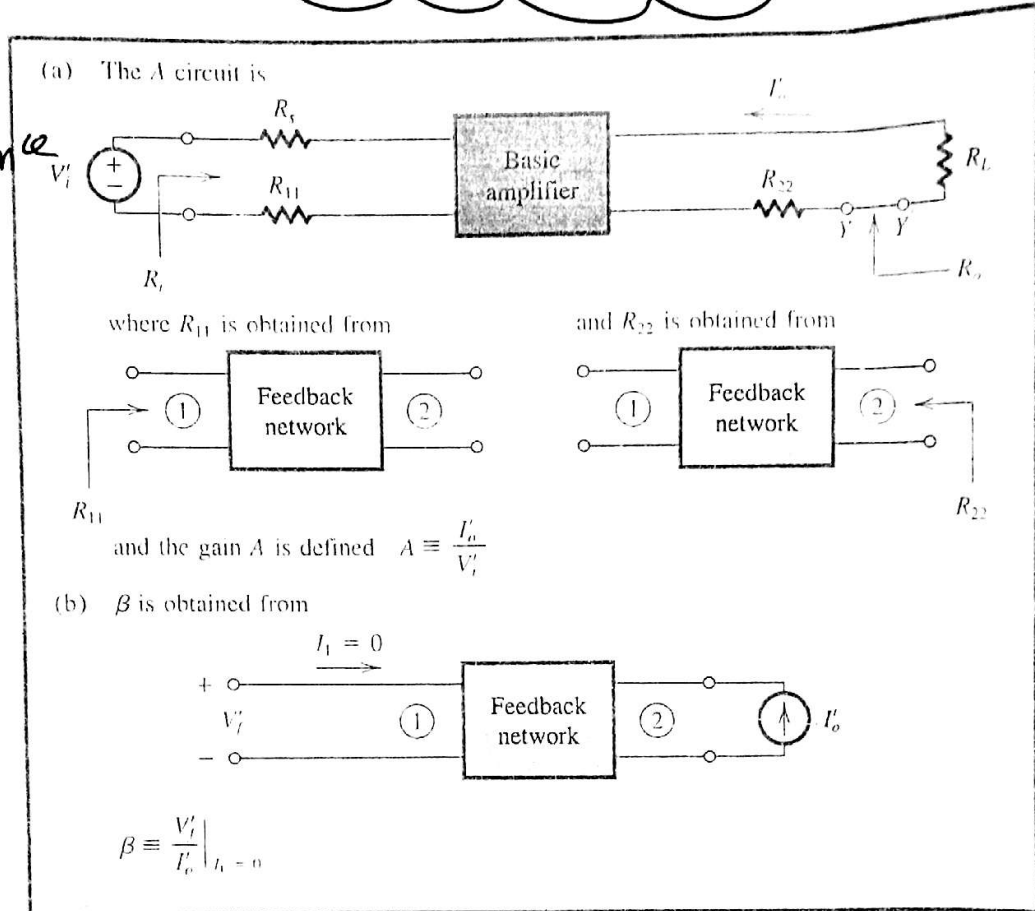


Fig. 8.16 Finding the A circuit and β for the current-sampling series-mixing (series-series) case.

Summary

For future reference we present in Fig. 8.16 a summary of the rules for finding A and β for a given series-series feedback amplifier of the type shown in Fig. 8.15(a). Note that R_i is the input resistance of the A circuit, and its output resistance is R_o , which can be determined by breaking the output loop and looking between Y and Y' . R_i and R_o can be used in Eqs. (8.16) and (8.18) to determine R_{if} and R_{of} (see Fig. 8.15b). The input and output resistances of the feedback amplifier can then be found by subtracting R_s from R_{if} and R_L from R_{of} .

$$R_{in} = R_{if} - R_s$$

$$R_{out} = R_{of} - R_L$$

EXAMPLE 8.2

Because negative feedback extends the amplifier bandwidth, it is commonly used in the design of broadband amplifiers. One such amplifier is the MC1553. Part of the circuit of

the MC1553 is shown in Fig. 8.17(a). The circuit shown (called a *feedback triple*) is composed of three gain stages with series-series feedback provided by the network composed of R_{E1} , R_F , and R_{E2} . Assume that the bias circuit, which is not shown, causes $I_{C1} = 0.6$ mA, $I_{C2} = 1$ mA, and $I_{C3} = 4$ mA. Using these values and assuming $h_{fe} = 100$ and $r_o = \infty$, find the open-loop gain A , the feedback factor β , the closed loop gain $A_f \equiv I_o/V_s$, the voltage gain V_o/V_s , the input resistance $R_{in} = R_{if}$, and the output resistance R_{of} (between nodes Y and Y' , as indicated). Now, if r_o of Q_3 is 25 k Ω , estimate an approximate value of the output resistance R_{out} .

SOLUTION

Employing the loading rules given in Fig. 8.16, we obtain the A circuit shown in Fig. 8.17(b). To find $A \equiv I_o/V_i$ we first determine the gain of the first stage. This can be written by inspection as

$$\frac{V_{c1}}{V_i} = \frac{-\alpha_1(R_{C1} // r_{\pi 2})}{r_{e1} + [R_{E1} // (R_F + R_{E2})]}$$

Since Q_1 is biased at 0.6 mA, $r_{e1} = 41.7 \Omega$. Transistor Q_2 is biased as 1 mA; thus $r_{\pi 2} = h_{fe}/g_{m2} = 100/40 = 2.5$ k Ω . Substituting these values together with $\alpha_1 = 0.99$, $R_{C1} = 9$ k Ω , $R_{E1} = 100 \Omega$, $R_F = 640 \Omega$, and $R_{E2} = 100 \Omega$ results in

$$\frac{V_{c1}}{V_i} = -14.92 \text{ V/V}$$

Next, we determine the gain of the second stage, which can be written by inspection as (note that $V_{b2} = V_{c1}$)

$$\frac{V_{c2}}{V_{c1}} = -g_{m2}[R_{C2} // (h_{fe} + 1)[r_{e3} + (R_{E2} // (R_F + R_{E1}))]]$$

Substituting $g_{m2} = 40$ mA/V, $R_{C2} = 5$ k Ω , $h_{fe} = 100$, $r_{e3} = 25/4 = 6.25 \Omega$, $R_{E2} = 100 \Omega$, $R_F = 640 \Omega$, and $R_{E1} = 100 \Omega$, results in

$$\frac{V_{c2}}{V_{c1}} = -131.2 \text{ V/V}$$


Finally, for the third stage we can write by inspection

$$\begin{aligned} \frac{I_o}{V_{c2}} &= \frac{I_{e3}}{V_{b3}} = \frac{1}{r_{e3} + (R_{E2} // (R_F + R_{E1}))} \\ &= \frac{1}{6.25 + (100 // 740)} = 10.6 \text{ mA/V} \end{aligned}$$


Combining the gains of the three stages results in

$$\begin{aligned} A \equiv \frac{I_o}{V_i} &= -14.92 \times -131.2 \times 10.6 \times 10^{-3} \\ &= 20.7 \text{ A/V} \end{aligned}$$


7

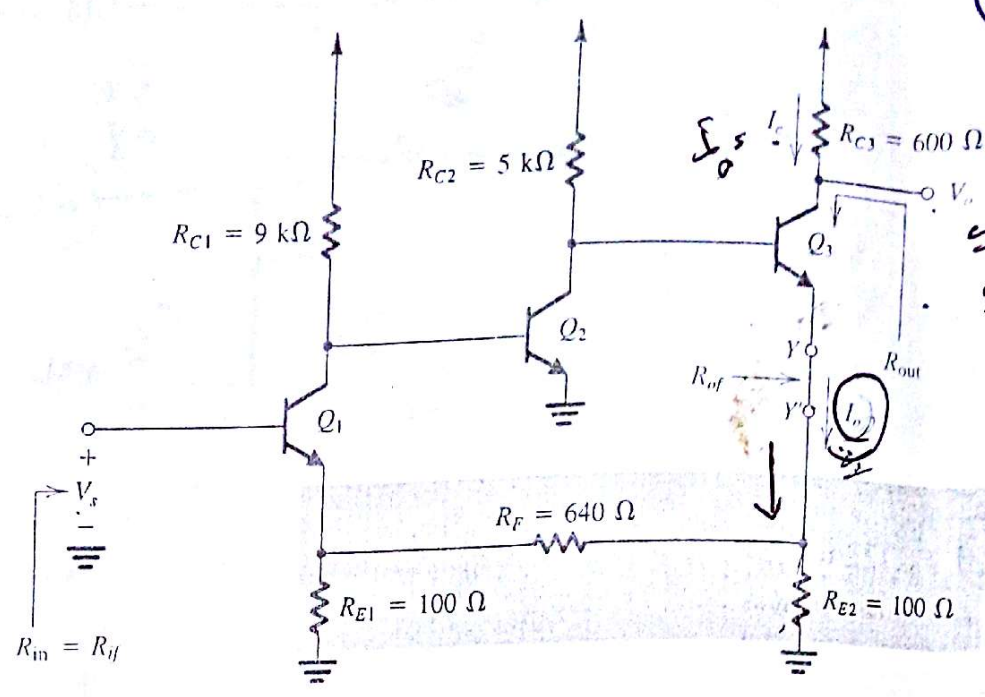


(a)

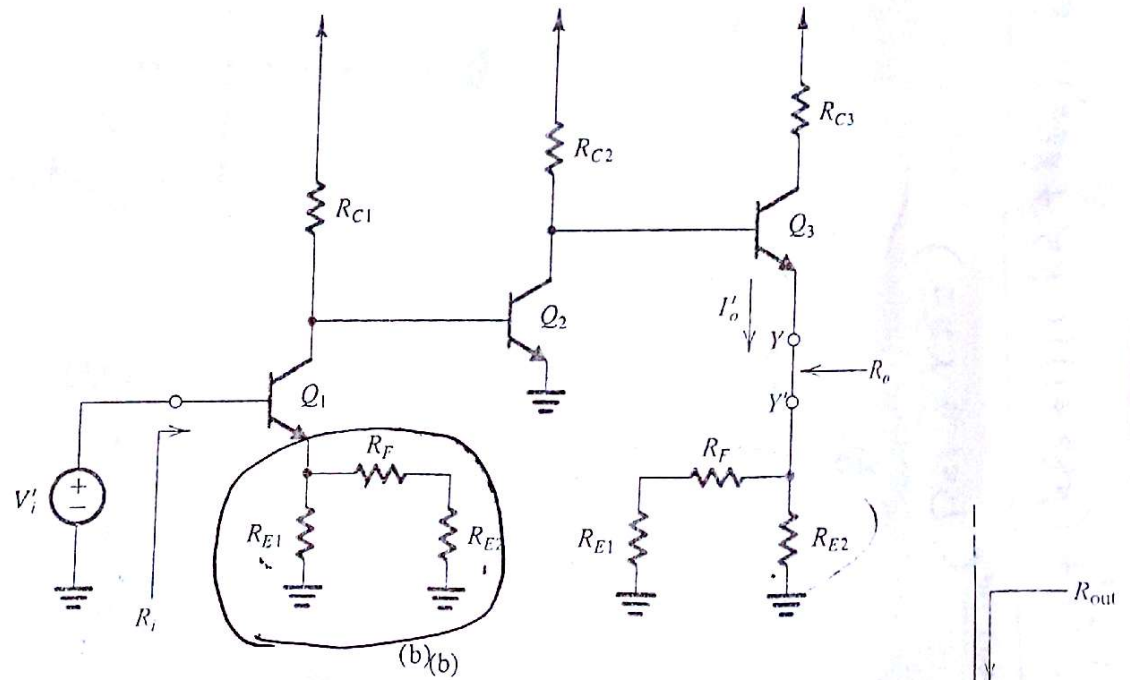

(b)

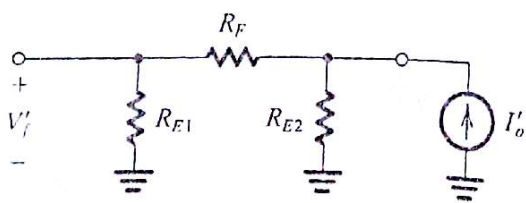

(c)

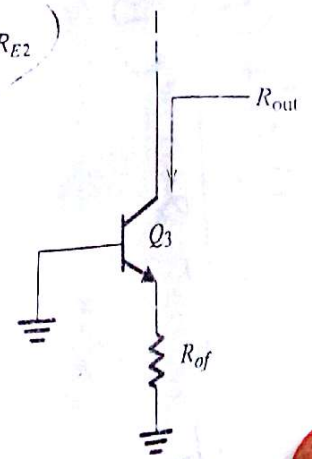


(d)

Fig. 8.17 Circuits for Example 8.2.

Model for the circuit

$$h_{fe} = \beta$$

(8)

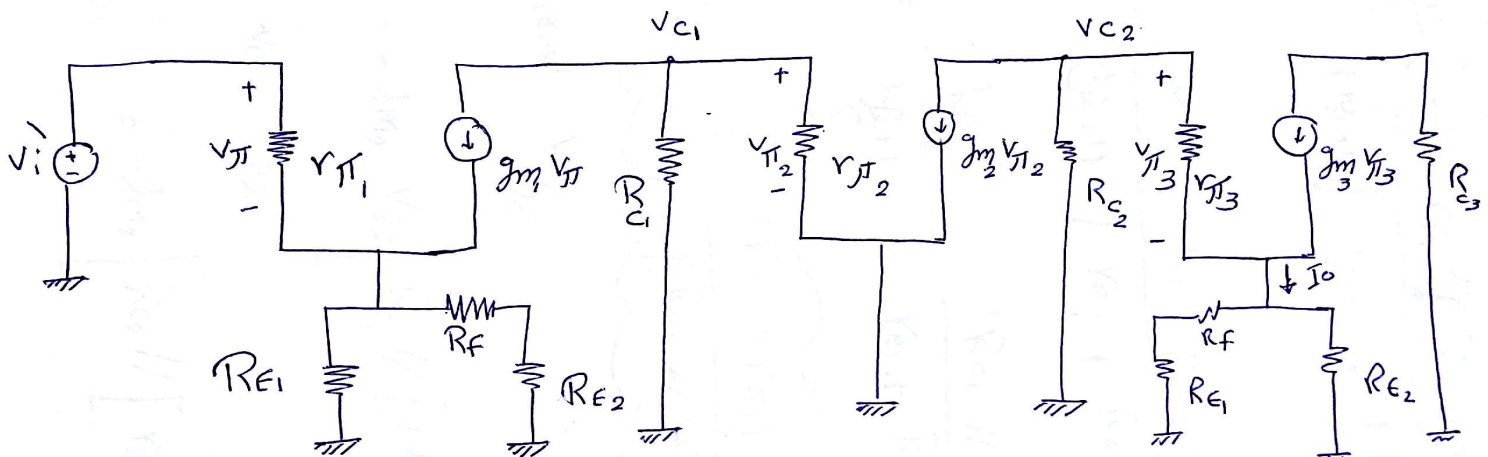

$$\therefore V_{C1} = -g_{m1} V_{\pi1} (R_{C1} \parallel r_{\pi2})$$

$$\text{and } V_i = i_b \left(r_{\pi1} + \frac{(h_{fe} + 1)}{\beta} (R_f + R_{E2}) \parallel R_{E1} \right)$$

$$r_{\pi} = \frac{\beta}{g_m}$$

$$r_e \approx \frac{1}{g_m} \approx \frac{r_{\pi}}{\beta}$$

$$r_{\pi} = (\beta + 1) r_e$$

$$\therefore \frac{V_{C1}}{V_i} = \frac{-g_{m1} (R_{C1} \parallel r_{\pi2})}{\frac{1}{r_{\pi1}} \left(r_{\pi1} + \frac{(h_{fe} + 1)}{\beta} (R_f + R_{E2}) \parallel R_{E1} \right)} = \frac{-g_{m1} r_{\pi1} (R_{C1} \parallel r_{\pi2})}{r_{\pi1} + (h_{fe} + 1) [R_{E1} \parallel (R_f + R_{E2})]}$$

$$\therefore \frac{V_{C1}}{V_i} = \frac{-g_{m1} r_{\pi 1} (R_{C1} \parallel r_{\pi 2})}{(h_{fe}+1) \left[\frac{r_{\pi 1}}{h_{fe}+1} + R_{E1} \parallel (R_F + R_{E2}) \right]} \quad (9)$$

$$= \frac{-\beta R_{C1} \parallel r_{\pi 2}}{(h_{fe}+1) [r_{e1} + R_{E1} \parallel (R_F + R_{E2})]}$$

$$= -\frac{h_{fe}}{h_{fe}+1} \frac{R_{C1} \parallel r_{\pi 2}}{r_{e1} + R_{E1} \parallel (R_F + R_{E2})}$$

$$\frac{V_{C1}}{V_i} = -\alpha \frac{(R_{C1} \parallel r_{\pi 2})}{r_{e1} + [R_{E1} \parallel (R_F + R_{E2})]}$$

and To find $\frac{V_{C2}}{V_{C1}}$

$$V_{C2} = -g_{m2} V_{\pi 2} \left[R_{C2} \parallel [r_{\pi 3} + (h_{fe}+1)(R_{E2} \parallel (R_F + R_{E1}))] \right]$$

and $V_{C1} = V_{\pi 2}$

$$\therefore \frac{V_{C2}}{V_{C1}} = -g_{m2} \left[R_{C2} \parallel [r_{\pi 3} + (h_{fe}+1)(R_F + R_{E1} \parallel R_{E2})] \right]$$

$$\frac{V_{c2}}{V_{c1}} = -g_{m2} \left[R_{c2} // \left[(h_{fe} + 1) \left[\frac{V_{\pi 3}}{h_{fe} + 1} + R_{E2} // (R_f + R_{E1}) \right] \right] \right]$$

$$= -g_{m2} \left[R_{c2} // (h_{fe} + 1) \left[r_{e3} + R_{E2} // (R_f + R_{E1}) \right] \right]$$

= ✓

$$\text{and } \frac{I_o}{V_{c2}} = \frac{I_{e3}}{V_{b3}} = \frac{g_{m3} V_{\pi 3} + V_{\pi 3}}{\cancel{\phantom{V_{\pi 3}}}}$$

$$I_{e3} = g_{m3} V_{\pi 3} + I_{b3}$$

$$= g_{m3} V_{\pi 3} + I_{b3}$$

$$\therefore \frac{I_o'}{V_{c2}} = \frac{1}{r_{e3} + (R_{E2} // (R_f + R_{E1}))}$$

$$\text{and } A = \frac{I_o'}{V_i} = \frac{V_{c1}}{V_i'} * \frac{V_{c2}}{V_{c1}} * \frac{I_o'}{V_{c2}}$$

= ✓

The circuit for determining the feedback factor β is shown in Fig. 8.17(c), from which we find

$$\begin{aligned}\beta &\equiv \frac{V_f'}{I_o'} = \frac{R_{E2}}{R_{E2} + R_F + R_{E1}} \times R_{E1} \\ &= \frac{100}{100 + 640 + 100} \times 100 = 11.9 \Omega\end{aligned}$$

The closed-loop gain A_f can now be found from

$$\begin{aligned}A_f &\equiv \frac{I_o}{V_s} = \frac{A}{1 + A\beta} \\ &= \frac{20.7}{1 + 20.7 \times 11.9} = 83.7 \text{ mA/V}\end{aligned}$$

The voltage gain is found from

$$\begin{aligned}\frac{V_o}{V_s} &= \frac{-I_o R_{C3}}{V_s} \approx -A_f R_{C3} \\ &= -83.7 \times 10^{-3} \times 600 = -50.2 \text{ V/V}\end{aligned}$$

The input resistance of the feedback amplifier is given by

$$R_{if} = R_i(1 + A\beta)$$

where R_i is the input resistance of the A circuit. The value of R_i can be found from the circuit in Fig. 8.17(b) as follows:

$$\begin{aligned}R_i &= (h_{fe} + 1)[r_{e1} + (R_{E1} \parallel (R_F + R_{E2}))] \\ &= 13.65 \text{ k}\Omega\end{aligned}$$

Thus,

$$R_{if} = 13.65(1 + 20.5 \times 11.9) = 3.34 \text{ M}\Omega$$

To find the output resistance R_o of the A circuit in Fig. 8.17(b), we break the circuit between Y and Y' . The resistance looking between these two nodes can be found to be

$$R_o = [R_{E2} \parallel (R_F + R_{E1})] + r_{e3} + \frac{R_{C2}}{h_{fe} + 1}$$

which, for the values given, yields $R_o = 143.9 \Omega$. The output resistance R_{of} of the feedback amplifier can now be found as

$$R_{of} = R_o(1 + A\beta) = 143.9(1 + 20.7 \times 11.9) = 35.6 \text{ k}\Omega$$

Note that the feedback stabilizes the emitter current of Q_3 , and thus the output resistance that is determined by the feedback formula is the resistance of the emitter loop (i.e., between Y and Y'), which we have just found, and not the resistance looking into the collector² of Q_3 . This is because the output resistance r_o of Q_3 is in effect outside the feedback loop. We

² This important point was first brought to the authors' attention by Gordon Roberts (see Roberts and Sedra, 1992).

shunt-shunt f.B

(12)

Trans-Resistance Amplifier

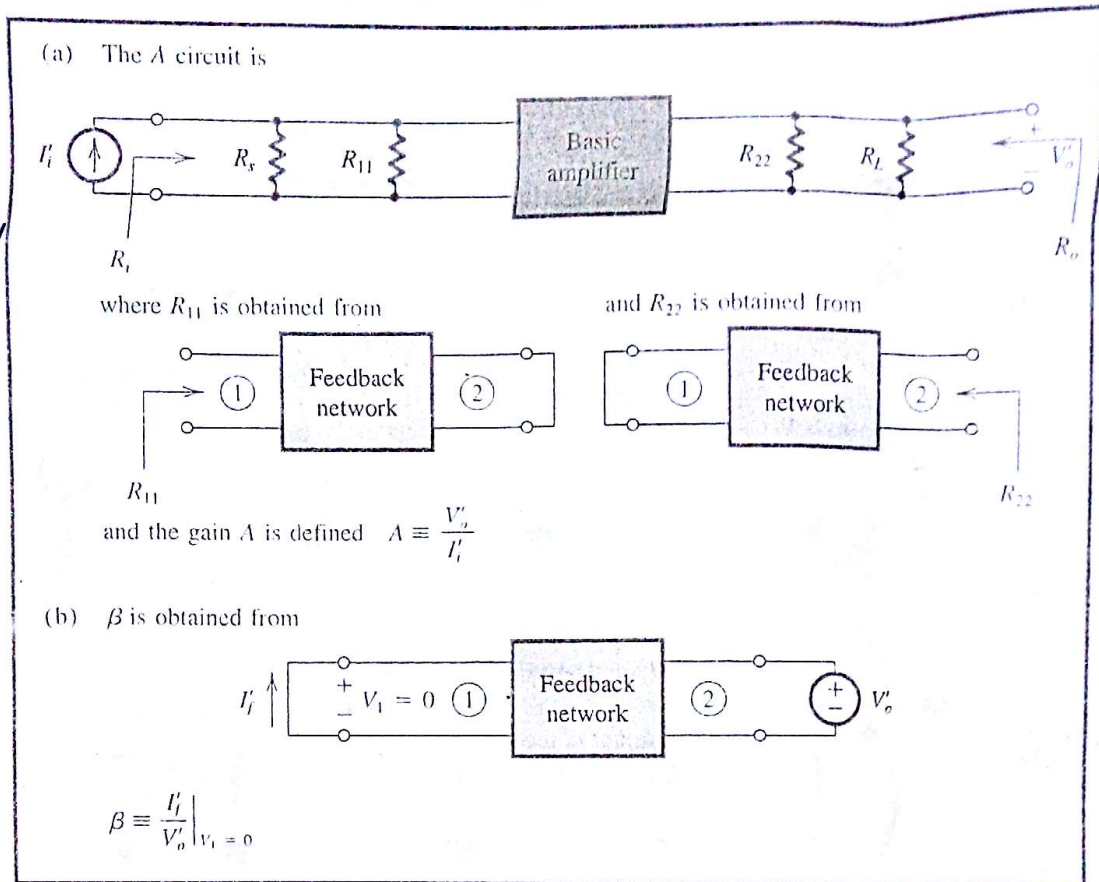


Fig. 8.20 Finding the A circuit and β for the voltage-sampling shunt-mixing (shunt-shunt) case.

(For the definition of the y parameters, refer to Appendix B.) Finally, we note that once R_{if} and R_{of} are determined using the feedback formulas (Eqs. 8.21 and 8.22), the input and output resistances of the amplifier proper (see definitions in Fig. 8.19) can be obtained as,

$$R_{in} = 1 / \left(\frac{1}{R_{if}} - \frac{1}{R_s} \right)$$

$$R_{out} = 1 / \left(\frac{1}{R_{of}} - \frac{1}{R_L} \right)$$

EXAMPLE 8.3

We want to analyze the circuit of Fig. 8.21(a) to determine the small-signal voltage gain V_o/V_s , the input resistance R_{in} , and the output resistance $R_{out} = R_{of}$. The transistor has $\beta = 100$.

8.6 THE SHUNT-SHUNT AND THE SHUNT-SERIES FEEDBACK AMPLIFIERS

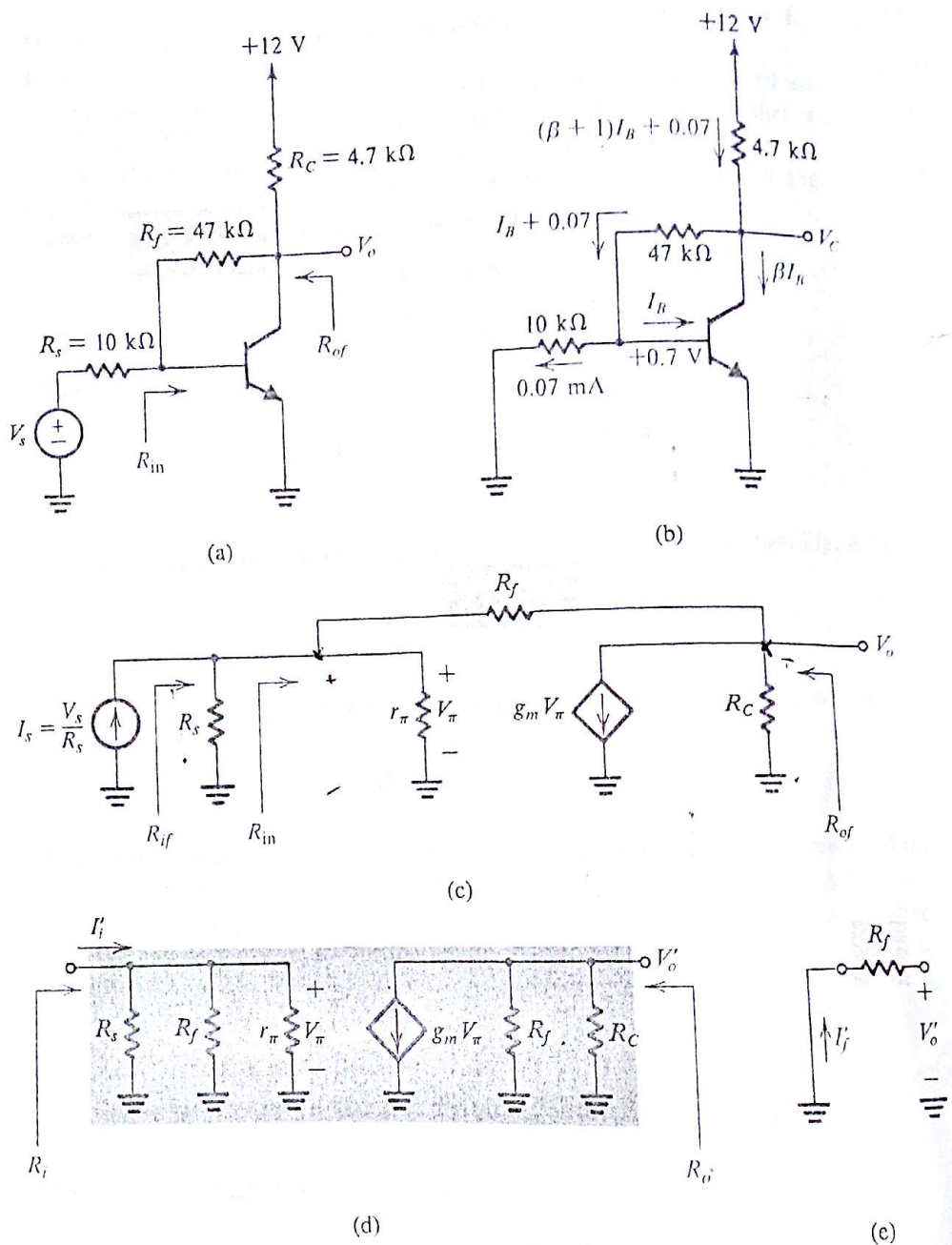


Fig. 8.21 Circuits for Example 8.3.

SOLUTION

First we determine the transistor dc operating point. The dc analysis is illustrated in Fig. 8.21(b), from which we can write

$$V_C = 0.7 + (I_B + 0.07)47 = 3.99 + 47I_B \quad \text{and} \quad \frac{12 - V_C}{4.7} = (\beta + 1)I_B + 0.07$$

These two equations can be solved to obtain $I_B \approx 0.015 \text{ mA}$, $I_C \approx 1.5 \text{ mA}$, and $V_C = 4.7 \text{ V}$.

To carry out small-signal analysis we first recognize that the feedback is provided by R_f , which samples the output voltage V_o and feeds back a current that is mixed with the source current. Thus it is convenient to use the Norton source representation, as shown in Fig. 8.21(c). The A circuit can be easily obtained using the rules of Fig. 8.20, and it is shown in Fig. 8.21(d). For the A circuit we can write by inspection

$$V_\pi = I_i'(R_s // R_f // r_\pi)$$

$$V_o' = -g_m V_\pi (R_f // R_C)$$

Thus

$$\begin{aligned} A = \frac{V_o'}{I_i'} &= -g_m (R_f // R_C) (R_s // R_f // r_\pi) \\ &= -358.7 \text{ k}\Omega \end{aligned}$$

The input and output resistances of the A circuit can be obtained from Fig. 8.21(d) as

$$R_i = R_s // R_f // r_\pi = 1.4 \text{ k}\Omega$$

$$R_o = R_C // R_f = 4.27 \text{ k}\Omega$$

The circuit for determining β is shown in Fig. 8.21(e), from which we obtain

$$\beta \equiv \frac{I_f'}{V_o'} = -\frac{1}{R_f} = -\frac{1}{47 \text{ k}\Omega}$$

Note that as usual the reference direction for I_f has been selected so that I_f subtracts from I_s . The resulting negative sign of β should cause no concern, since A is also negative, keeping the loop gain $A\beta$ positive, as it should be for the feedback to be negative.

We can now obtain A_f (for the circuit in Fig. 8.21c) as

$$A_f \equiv \frac{V_o}{I_s} = \frac{A}{1 + A\beta}$$

$$\frac{V_o}{I_s} = \frac{-358.7}{1 + 358.7/47} = \frac{-358.7}{8.63} = -41.6 \text{ k}\Omega$$

To find the voltage gain V_o/V_s we note that

$$V_s = I_s R_s$$

Thus

$$\frac{V_o}{V_s} = \frac{V_o}{I_s R_s} = \frac{-41.6}{10} = -4.16 \text{ V/V}$$

The input resistance with feedback (see Fig. 8.21c) is given by

$$R_{if} = \frac{R_i}{1 + A\beta}$$

(15)

Thus

$$R_{if} = \frac{1.4}{8.63} = 162.2 \Omega$$

This is the resistance seen by the current source I_s in Fig. 8.21(c). To obtain the input resistance of the feedback amplifier excluding R_s (that is, the required resistance R_{in}) we subtract $1/R_s$ from $1/R_{if}$ and invert the result; thus $R_{in} = 165 \Omega$. Finally, the amplifier output resistance R_{of} is evaluated using

$$R_{of} = \frac{R_o}{1 + A\beta} = \frac{4.27}{8.63} = 495 \Omega$$

An Important Note

The method we have been employing for the analysis of feedback amplifiers is predicated on two premises: Most of the forward transmission occurs in the basic amplifier, and most of the reverse transmission (feedback) occurs in the feedback network. For each of the three topologies considered thus far, these two assumptions were mathematically expressed as conditions on the relative magnitudes of the forward and reverse two-port parameters of the basic amplifier and the feedback network. Since the circuit considered in Example 8.3 is simple, we have a good opportunity to check the validity of these assumptions.

Reference to Fig. 8.21(d) indicates clearly that the basic amplifier is unilateral; thus *all* of the reverse transmission takes place in the feedback network. The case with forward transmission, however, is not so clear, and we must evaluate the forward y parameters. For the A circuit in Fig. 8.21(d), $y_{21} = g_m$. For the feedback network it can be easily shown that $y_{21} = -1/R_f$. Thus for our analysis method to be valid we must have $g_m \gg 1/R_f$. For the numerical values in Example 8.3, $g_m = 60 \text{ mA/V}$ and $1/R_f = 0.02 \text{ mA/V}$, indicating that this assumption is more than justified. Nevertheless, in designing feedback amplifiers, care should be taken in choosing component values to ensure that the two basic assumptions are valid.

The Shunt-Series Configuration

Figure 8.22 shows the ideal structure of the shunt-series feedback amplifier. It is a current amplifier whose gain with feedback is defined as

$$A_f \equiv \frac{I_o}{I_s} = \frac{A}{1 + A\beta} \quad (8.23)$$

The input resistance with feedback is the resistance seen by the current source I_s and is given by


$$R_{if} = \frac{R_i}{1 + A\beta} \quad (8.24)$$

Again we note that the shunt connection at the input reduces the input resistance. The output resistance with feedback is the resistance seen by breaking the output circuit, such as between O and O' , and looking between the two terminals thus generated (that is, between O


shunt-series P.B

16


(a) The A circuit is

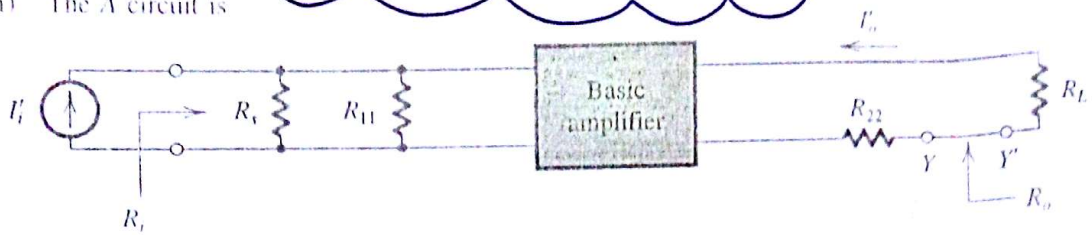

where R_{11} is obtained from

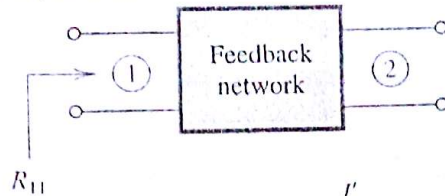


and R_{22} is obtained from

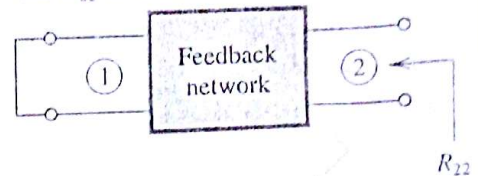

and the gain A is defined as $A \equiv \frac{I_o}{I_i}$

(b) β is obtained from

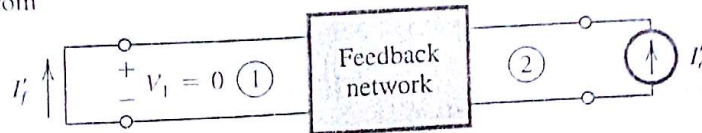

$$\beta \equiv \frac{I_i}{I_o} \Big|_{V_1 = 0}$$

Fig. 8.24 Finding the A circuit and β for the current-sampling shunt-mixing (shunt-series) case.

(For the definition of the g parameters refer to Appendix B.) Finally, we note that once R_{if} and R_{of} have been determined using the feedback equations (Eqs. 8.24 and 8.25), the input and output resistances of the amplifier proper, R_{in} and R_{out} (Fig. 8.23), can be found as

$$R_{in} = 1 \Big/ \left(\frac{1}{R_{if}} - \frac{1}{R_s} \right)$$

$$R_{out} = R_{of} - R_L$$

EXAMPLE 8.4

Figure 8.25 shows a feedback circuit of the shunt-series type. Find I_{out}/I_{in} , R_{in} , and R_{out} . Assume the transistors to have $\beta = 100$ and $V_A = 75$ V.

SOLUTION

We begin by determining the dc operating points. In this regard we note that the feedback signal is capacitively coupled; thus the feedback has no effect on dc bias. Neglecting the

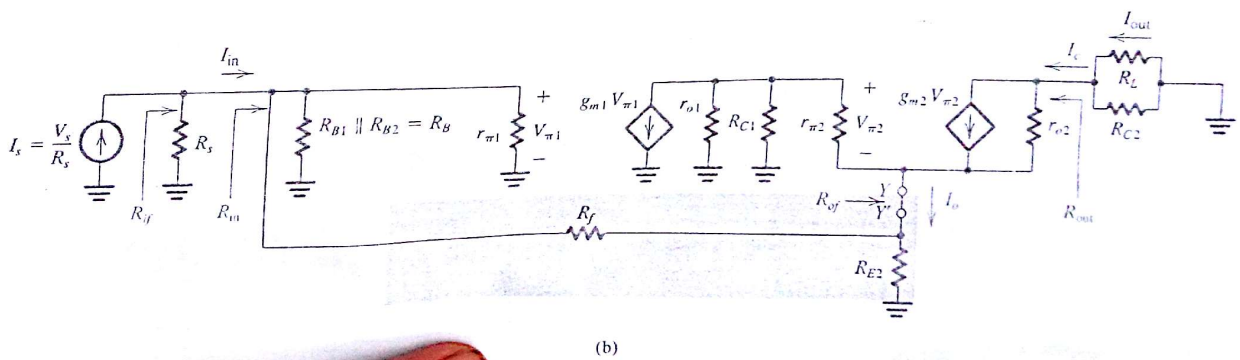
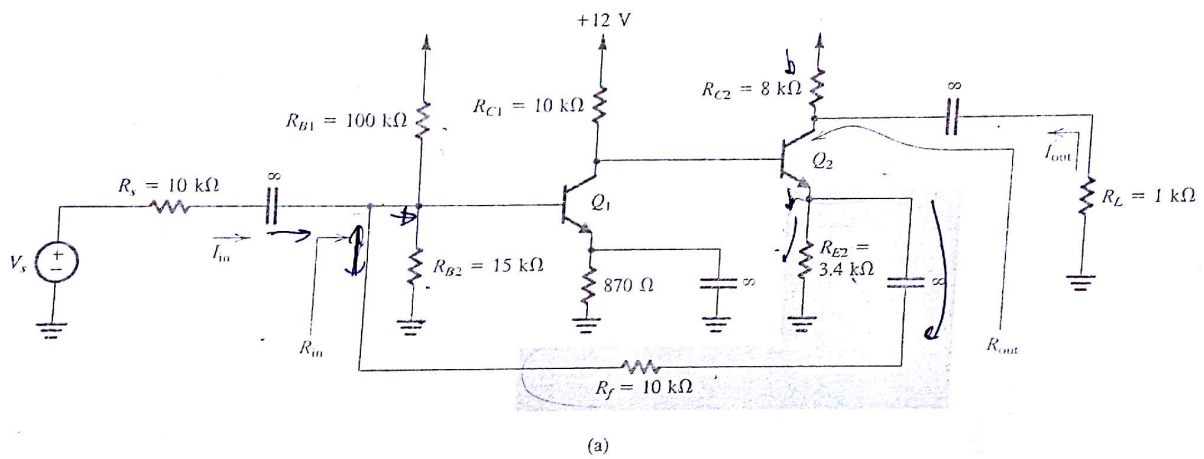


Fig. 8.25 Circuits for Example 8.4.

effect of finite transistor β and V_A , the dc analysis proceeds as follows:

$$V_{B1} \approx 12 \frac{15}{100 + 15} = 1.57 \text{ V}$$

$$V_{E1} \approx 1.57 - 0.7 = 0.87 \text{ V}$$

$$I_{E1} = 0.87/0.87 = 1 \text{ mA}$$

$$V_{C1} \approx 12 - 10 \times 1 = 2 \text{ V}$$

$$V_{E2} \approx 2 - 0.7 = 1.3 \text{ V}$$

$$I_{E2} \approx 1.3/3.4 \approx 0.4 \text{ mA}$$

$$V_{C2} \approx 12 - 0.4 \times 8 = 8.8 \text{ V}$$

The amplifier equivalent circuit is shown in Fig. 8.25(b), from which we note that the feedback network is composed of R_{E2} and R_f . The feedback network samples the emitter current of Q_2 , I_o , which is approximately equal to the collector current I_c . Also note that the required current gain, I_{out}/I_{in} , will be slightly different than the closed-loop current gain $A_f \equiv I_o/I_s$.

The A circuit is shown in Fig. 8.25(c), where we have obtained the loading effects of the feedback network using the rules of Fig. 8.24. For the A circuit we can write

$$V_{\pi 1} = I'_i [R_s // (R_{E2} + R_f) // R_B // r_{\pi 1}]$$

$$V_{b2} = -g_{m1} V_{\pi 1} \{r_{o1} // R_{C1} // [r_{\pi 2} + (\beta + 1)(R_{E2} // R_f)]\}$$

$$I'_o \approx \frac{V_{b2}}{r_{e2} + (R_{E2} // R_f)}$$

where we have neglected the effect of r_{o2} . These equations can be combined to obtain the open-loop current gain A,

$$A \equiv \frac{I'_o}{I'_i} \approx -201.45 \text{ A/A}$$

The input resistance R_i is given by

$$R_i = R_s // (R_{E2} + R_f) // R_B // r_{\pi 1} = 1.535 \text{ k}\Omega$$

The output resistance R_o is that found by looking into the output loop of the A circuit between nodes Y and Y' (see Fig. 8.25c) with the input excitation I'_i set to zero. Neglecting the small effect of r_{o2} it can be shown that

$$\begin{aligned} R_o &= (R_{E2} // R_f) + r_{e2} + \frac{R_{C1} // r_{o1}}{\beta + 1} \\ &= 2.69 \text{ k}\Omega \end{aligned}$$

The circuit for determining β is shown in Fig. 8.25(d), from which we find

$$\beta \equiv \frac{I'_f}{I'_o} = -\frac{R_{E2}}{R_{E2} + R_f} = -\frac{3.4}{13.4} = -0.254$$

* what is feedback

Feedback.

المقصود بالفيديباك هو أخذ جزء من الخرج وبيتم ارجاعه مرة أخرى الى الدخل

-ve feedback

← الـ 180° موجب
الـ

+ve feedback

← الـ

-ve F.B
used in
amplifier


&

+ve F.B
used in
oscillators

-ve F.B → feedback signal is out of phase of 180°
phase shift = 180°

+ve F.B → " " " " in phase " "
phase shift = 0°

* The General feedback structure

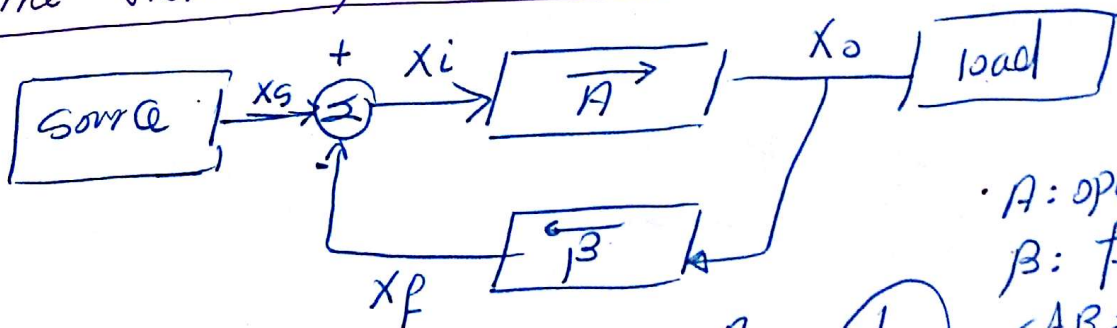

• A: open loop Gain
β: feedback parameter
AB: Loop Gain

$$A_f = \frac{A}{1 + A\beta} \quad A\beta \gg 1 \quad \approx \frac{A}{A\beta} \approx \left(\frac{1}{\beta} \right)$$

* feedback types There are 4 types of feedback

↳ series-shunt

↳ series-series

↳ shunt-shunt

↳ shunt-series



↓

↓

input الـ

output الـ

Series - Shunt Feedback

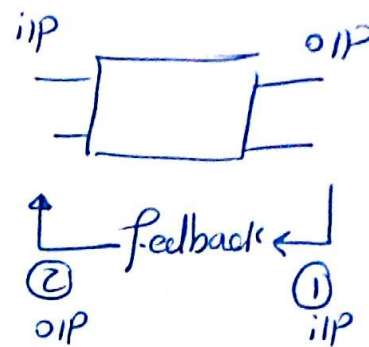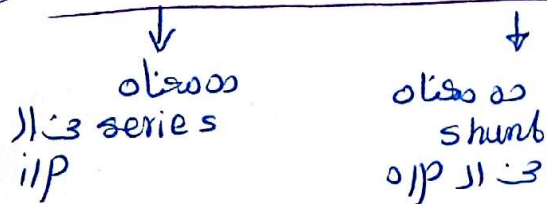

عند (1)

Current feedback \equiv Series \leftarrow لذلك تسمى i/p

عند (2) عادة عمل feedback لتيار الخرج
: تواتر هافز I_o

Voltage feedback \equiv Parallel \leftarrow لذلك تسمى o/p

عادة عمل feedback لجهد الخرج
: تواتر هافز V_o

عند (2)

عادة ادخل feedback على اتيار

Called shunt

لتيار في الدخل : ادخلنا تواتر في نقطة الدخل

Called series

لجهد في الدخل : ادخلنا تواتر مع الدخل

Series - Series
↑ ↑

يدخل على اتيار
جهد في الدخل
لافز التيار
تفاع الخرج

Series - Shunt
↑ ↑

ادخل على اتيار
جهد في الا i/p
لافز جهد
الخرج

في المعاضه
analysis
افياء

model, R_{i1}, R_{o1}, A, β
+ R_{i1}, R_{22}

[1] -ve F-B, $A = 10^5$ "open loop gain" $A_f = 100$ Find feedback factor β ??

manu factoring error in $A \rightarrow A_{new} = 10^3$

what is the closed loop gain

what is the % change in A_f

$$A_f = \frac{A}{1+A\beta} \rightarrow A\beta = \frac{A}{A_f} - 1 = \frac{10^5}{100} - 1 = 999$$

$$\beta = \frac{999}{10^5} = 9.99 \times 10^{-3} \#$$

$$\text{at } A = 10^3 \rightarrow A_f = \frac{A}{1+A\beta} = \frac{10^3}{1 + 10^3 \times (9.99 \times 10^{-3})}$$

$$A_f = 90.99$$

$$\frac{\Delta A_f}{A_f} = \frac{A_{f_{new}} - A_{f_{old}}}{A_{f_{old}}} = \frac{90.99 - 100}{100} \times 100 = -9\% \#$$

[2] -ve F-B, Find loop gain $A\beta$, sensitivity of $\frac{\text{Closed loop gain}}{\text{open loop gain}} = -20 \text{ dB}$

become $\frac{1}{2}$

$$\frac{\frac{\Delta A_f}{A_f}}{\frac{\Delta A}{A}} = \frac{1}{1+A\beta} = \text{sensitivity} = -20 \text{ dB}$$

$$= 1+A\beta = 20 \text{ dB}$$

$$20 \log(1+A\beta) \Big|_{\text{ratio}} = 20 \text{ dB}$$

$$1+A\beta = 10$$

$$A\beta = 9 \#$$

$$\frac{1}{1+A\beta} = \frac{1}{2}$$

$$1+A\beta = 2$$

$$A\beta = 1 \#$$

amplifier has particular non linear CLC

can be approximated as follows

- For small signal $\rightarrow |V_i| < 10\text{mV} \rightarrow \frac{V_o}{V_i} = 10^3$

- for intermediate input signal $\rightarrow 10\text{mV} \leq |V_i| \leq 50\text{mV} \rightarrow \frac{V_o}{V_i} = 10^2$

for large signal $\rightarrow |V_i| \geq 50\text{mV}$

• The amplifier connected in $-ve$ F.B \rightarrow Final β

Feedback factor ??
that reduce the factor of gain to only 10% change (at $V_i = 10\text{mV}$)

• what is the CLC of amplifier with F.B ??

reduce = 10%
remain = 90%

$$A_{f2} = 0.9 A_{f1}$$

$$\frac{100}{1+100\beta} = 0.9 \frac{10^3}{1+10^3\beta} \rightarrow \beta = 0.08$$

$$A_f = \frac{A}{1+A\beta}$$

$$A_{f1} = \frac{10^3}{1+10^3(0.08)} = 12.84 \rightarrow |V_i| \leq 10\text{mV}$$

$$A_{f2} = \frac{10^2}{1+10^2(0.08)} = 10.1 \rightarrow 10\text{mV} \leq |V_i| \leq 50\text{mV}$$

then o/p saturated $\rightarrow |V_i| \geq 50\text{mV}$

A_{ov}

$$\frac{V_i}{A=10^3} \rightarrow \frac{V_i}{A=10^2}$$

Feedback

$$\frac{V_i}{A_f=12.4} \rightarrow \frac{V_i}{A_f=10}$$

معدل التغير في A_f أقل منه معدل تغير A

5) Series-shunt $f \cdot B$

amplifier \rightarrow i/p & o/p resistors = 1K

$$\text{Gain} = A = 2000 \text{ V/V}$$

feedback parameter $\beta = 0.1 \text{ V/V}$

Find A_f , i/p , o/p $R_{i/f}$ of $R_{o/f}$

$$A_f = \frac{A}{1 + A\beta} = \frac{2000}{1 + 2000 \times 0.1} \quad \#$$


$$R_{i/f} = R_i (1 + A\beta) = 1K [1 + 2000 \times 0.1] \quad \#$$

$$R_{o/f} = \frac{R_o}{1 + A\beta} = \frac{1K}{(1 + 2000 \times 0.1)} \quad \#$$

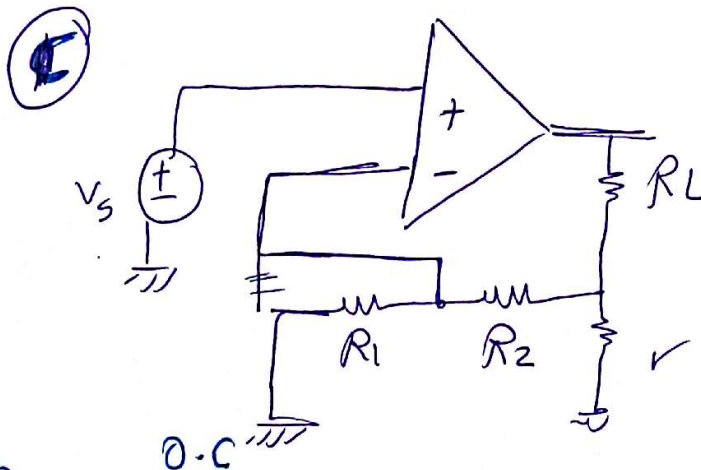5) for each of the following op-amp

\rightarrow identify feedback topology

\rightarrow find expression for β and then A_f



$R_L \Rightarrow$ open circuit

$I_f = 0 \quad \therefore$ Current Feedback

series \leftarrow o/p \therefore

ویرجی س کی ال i/p کی لقیات - : تو ال

Series-series $\#$


لتیید النوع
 \rightarrow put $R_L = o.c$
if the signal returned
to the amplifier i/p
by feedback = 0

\therefore Current feedback

\rightarrow put $R_L = s.c$

----- = 0

\therefore voltage feedback

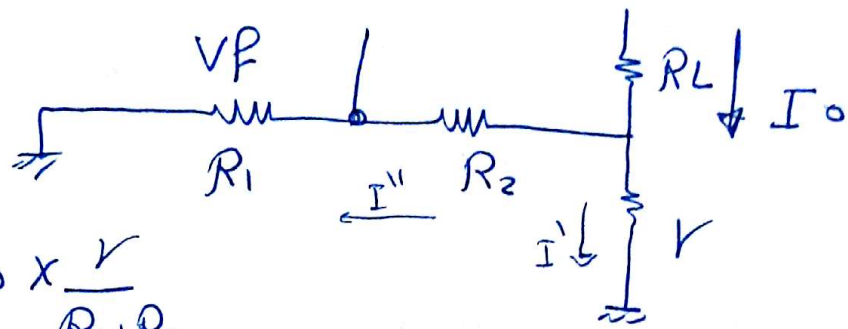


$$I'' = I_0 \times \frac{V}{R_1 + R_2}$$

$$V_F = I'' R_1 = \frac{I_0 V R_1}{R_1 + R_2}$$

$$\beta = \frac{V_F}{I_0} = \frac{V R_1}{R_1 + R_2} \neq$$

$$A_f \approx \frac{1}{\beta} = \neq \frac{R_1 + R_2}{V R_1} = \left[\frac{1}{V} + \frac{R_2}{V R_1} \right] \neq$$

(a)

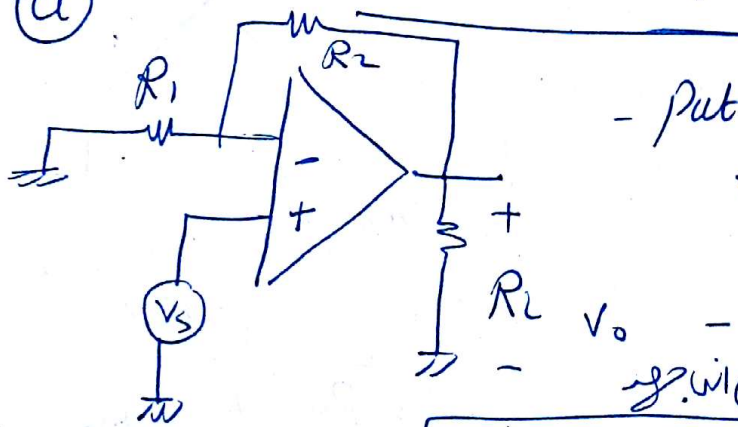


- put $R_L \Rightarrow S.C$
 $V_F = 0$

\rightarrow voltage feedback
 shunt \rightarrow o/p

V_o - voltage across R_L
 \rightarrow series in i/p

series-shunt

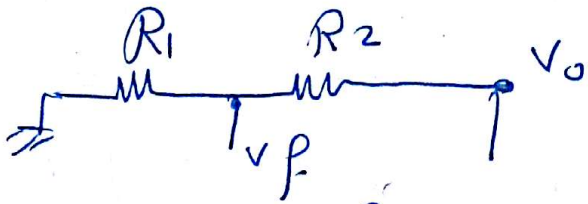

$$V_F = V_o \times \frac{R_1}{R_1 + R_2}$$

$$\frac{V_F}{V_o} = \beta = \frac{R_1}{R_1 + R_2} \neq$$

$$A \approx \frac{1}{\beta} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1} \neq$$


II

sec (2) Feed back

Series-shunt Feedback

↓
دور معنای
در ورودی
↓
دور معنای
در خروجی

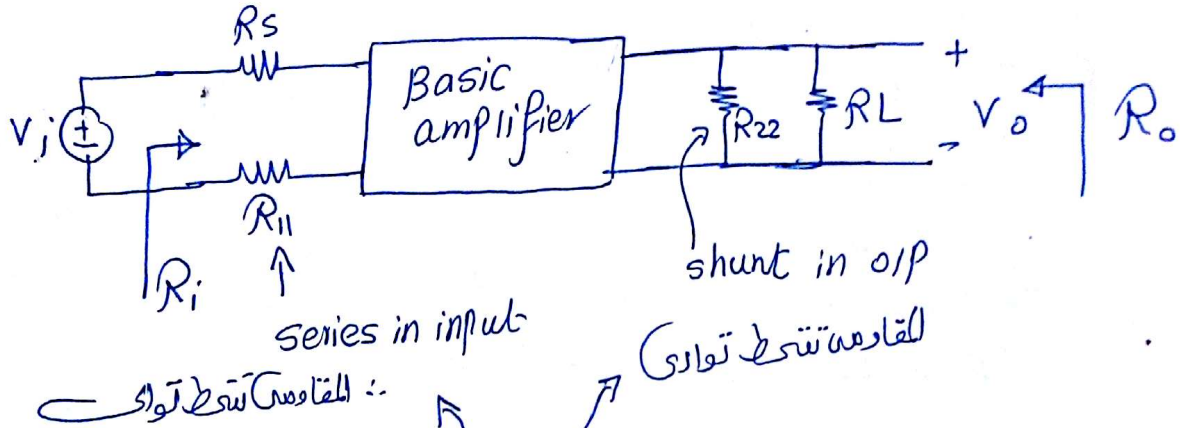i/p → o/p
A → voltage gain $A_v = \frac{V_o}{V_i}$





الایتن دقل نشیبت وجوده
Feed back circuit

	i/p	o/p
V	O.C	S.C
I	S.C	O.C

* To find R_{11}

* To find R_{22}

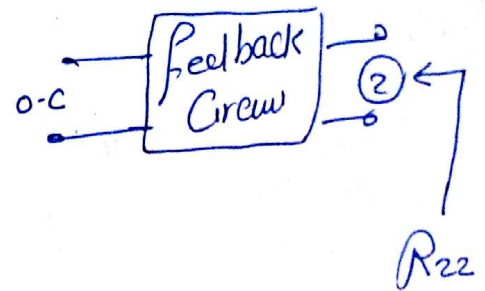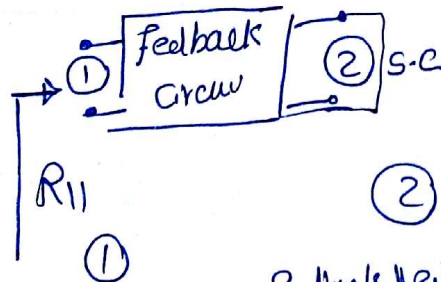

دقل الایتن
amplifier الایتن
دقل الایتن
amplifier الایتن

* To find β

$$\beta = \frac{V_f}{V_o}$$

i/p amplifier
i/p feedback
2 → shunt




Series. Series Feedback

دەستخاوە
فەانەن

دەستخاوە
فەانەن


فەانەن

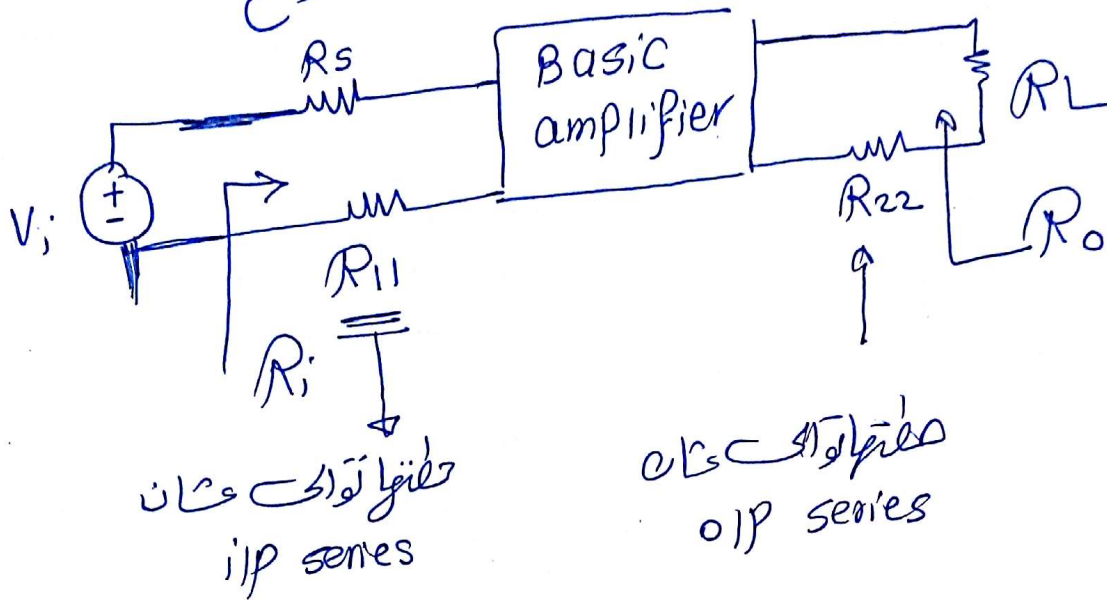


* $\frac{V_i}{I_o}$ \Rightarrow $\frac{V_o}{I_o}$

$$A \equiv \frac{I_o}{V_i} = \text{Transconductance.}$$

* To find R_{ii}

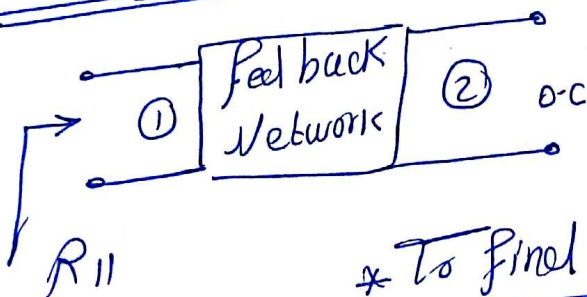

* To find R_{zz}

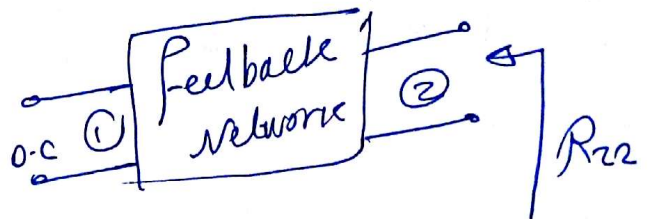

* To find β



$$\beta = \frac{V_p}{I_o}$$

* in Series-shunt

of A circuit
 R_s $\left\{ \begin{array}{l} R_i \& R_o \rightarrow \text{input \& output impedance} \\ R_{if} \& R_{of} \rightarrow \text{of feedback amplifier including } R_L \& R_s \end{array} \right.$

The actual input and output impedance of feedback amplifier excluding $R_L \& R_s$

$$R_{in} = R_{if} - R_s$$

$$R_{out} = \frac{1}{\frac{1}{R_{of}} - \frac{1}{R_L}}$$

* in series-series

$$R_{in} = R_{if} - R_s$$

$$R_{out} = R_{of} - R_L$$

[7] series-series feedback amplifier employs a transconductance
 $G_m = 100 \text{ mV/A}$ & i/p Resistance of $10 \text{ k}\Omega$
 o/p " " " $100 \text{ k}\Omega$

• feedback network $\rightarrow \beta = 0.1 \text{ V/mA}$
 and i/p resistance " with port 1 open circuit
 $= 100 \text{ k}\Omega$

$R_{\text{signal source}} = 10 \text{ k}\Omega$ $R_L = 10 \text{ k}\Omega$ $R_{22} = 10 \text{ k}\Omega$
 Find A_f & R_{in} & R_{out} R_{11}

[7] series-series feedback employs a trans conductance

- $G_m = 100 \text{ mV/A}$ i/p R of $10 \text{ k}\Omega$
o/p R of $100 \text{ k}\Omega$

- feedback network $\rightarrow \beta = 0.1 \text{ V/mA}$

i/p R " with port 1 open circuit = $100 \text{ k}\Omega$
i/p R " " " 2 " " " = $10 \text{ k}\Omega$

$R_s = 10 \text{ k}\Omega$

$R_L = 10 \text{ k}\Omega$

Find A_f & R_{in} & R_{out}

Solution

$$A_f = \frac{A}{1 + A\beta}$$

$R_{in} = R_{if} - R_s \quad \#$
series

$R_{if} = R_i (1 + A\beta)$

$R_i = R_s + R_{iamp} + R_{ii}$

$R_{out} = R_{of} - R_L \quad \#$
series

$R_{of} = R_o (1 + A\beta)$



$R_o = R_L + R_{oamp} + R_{22}$

- 9 a) identify F.B type
 b) Draw equivalent circuit of amplifier + feedback
 c) expression and calculate $A_v, \beta, A_f, R_{if}, R_o$

$R_L = R_S = 10k\Omega$

$g_m = 4mA/V$ $V_0 = 100\Omega$

$R_1 = 20k\Omega$ $R_2 = 20k\Omega$

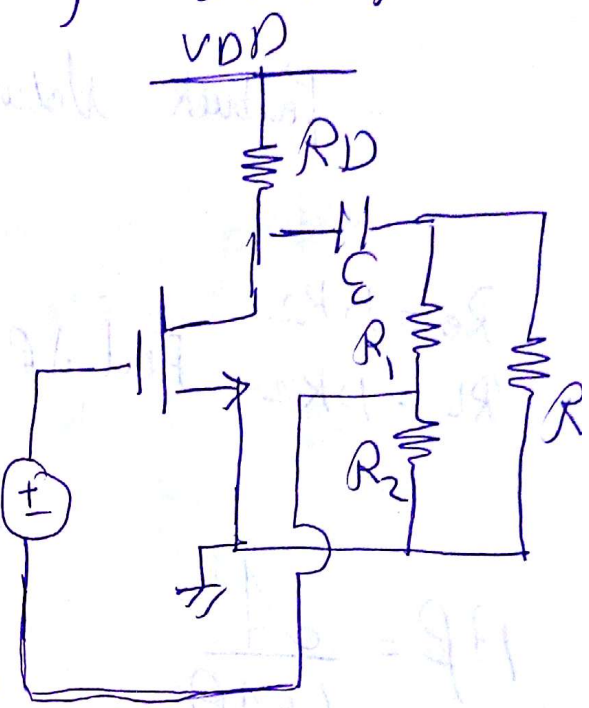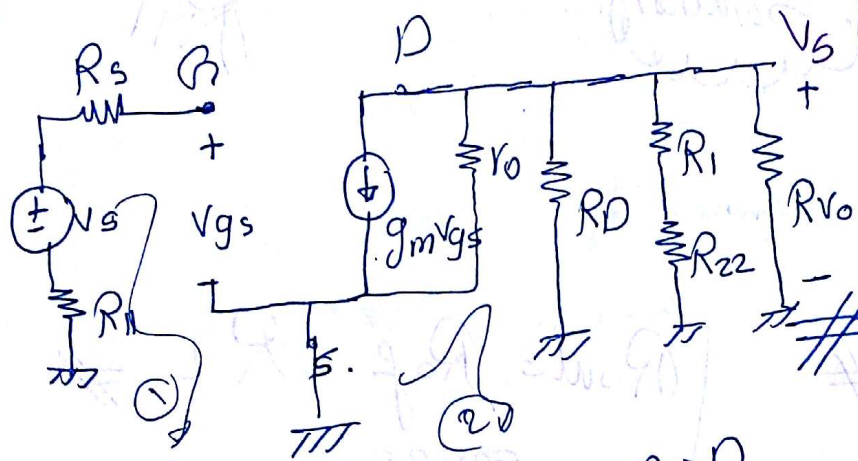

if $P \rightarrow$ Gate o/p $\rightarrow D$.
 Common-source

Series-shunt
 $\frac{V_o}{V_i}$ $\frac{V_o}{V_i}$

Note

$A_v = \text{voltage gain} = -g_m R_{\text{Drain}}$

- at K.V.L ①

$V_0 = -(g_m V_{gs}) [R_D \parallel (R_1 + R_{22}) \parallel R \parallel V_0]$

- at K.V.L ②

$V_{in} = +V_{gs}$

$A_v = \frac{V_0}{V_i} = \frac{-g_m V_{gs} [R_D \parallel (R_1 + R_{22}) \parallel R \parallel V_0]}{V_{gs}}$

$= -g_m [R_D \parallel (R_1 + R_{22}) \parallel R \parallel V_0]$

Mosfet

• with channel length modulation
 $(\lambda \neq 0)$
 $V_0 \rightarrow \infty$


• without channel length modulation
 $(\lambda = 0)$
 $V_0 \rightarrow \infty$

BJT

with early effect $V_A \neq \infty$
 without " " $V_A \rightarrow \infty$

$$R_i = R_{i1} + R_s + \infty = \infty \neq$$
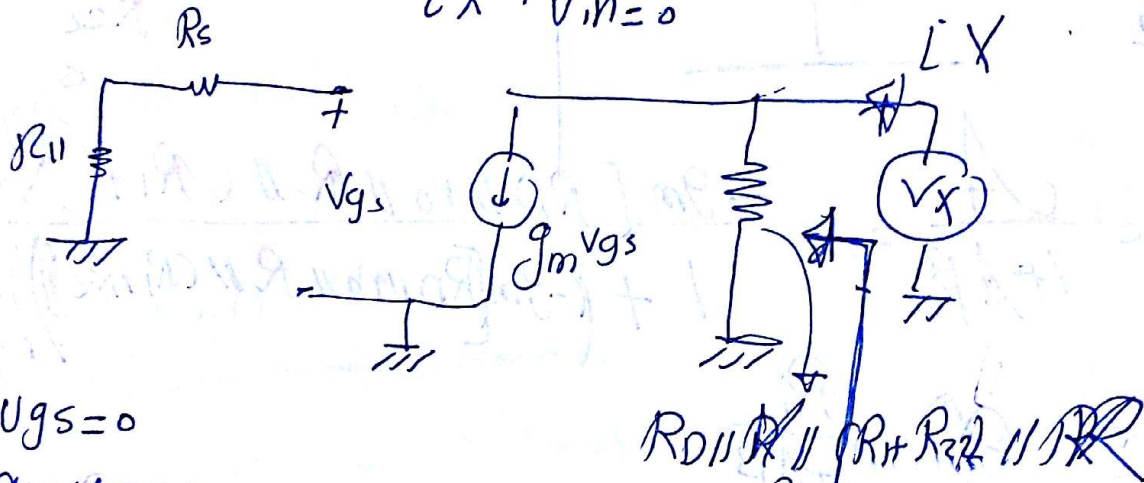
$$R_o \rightarrow R_o = \frac{V_X}{I_X} \mid V_{in} = 0$$



$$V_{gs} = 0$$

$$g_m V_{gs} = 0 \rightarrow 0-C$$

$$R_o = R_D \parallel R \parallel (R_1 + R_{eq}) \neq R_o$$

feedback سلسله شنت

$$A_f = \frac{A}{1+A\beta}$$


series-shunt

$$R_{if} = R_i / (1+A\beta)$$

$$R_{of} = \frac{R_o}{1+A\beta}$$

$$\frac{j\omega R_i}{1+A\beta} \text{ series } \frac{j\omega R_o}{1+A\beta}$$

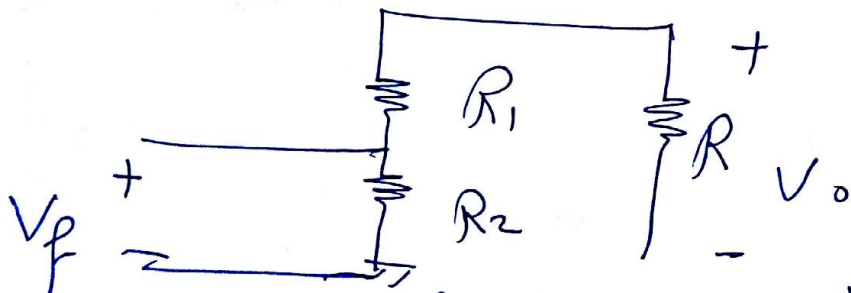
$$R_{22} \& R_{11} \& \beta \text{ } j\omega L_c \text{ } Z_{out}$$



$$V_f = V_o \times \frac{R_2}{R_1 + R_2}$$

$$\beta = \frac{V_f}{V_o} = \frac{R_2}{R_1 + R_2}$$

R_{22}

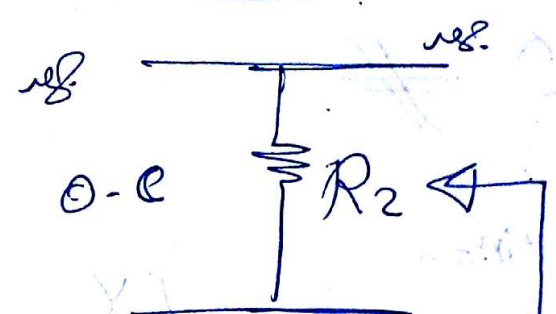

$R_{22} = R_2$


$$\therefore A_f = \frac{A}{1+A\beta} = \frac{-g_m [R_D \parallel r_o \parallel R \parallel (R_1 + R_2)]}{1 + (-g_m [R_D \parallel r_o \parallel R \parallel (R_1 + R_2)]) \frac{R_2}{R_1 + R_2}}$$

$R_{if} = \infty \cdot \frac{R_i}{1+A\beta}$

$$R_{of} = \frac{R_o}{1+A\beta} = \frac{R_D \parallel r_o \parallel R \parallel (R_1 + R_2)}{1 + (-g_m [R_D \parallel r_o \parallel R \parallel (R_1 + R_2)]) \frac{R_2}{R_1 + R_2}}$$

$R_{in} \& R_{out} \text{ is } \neq$

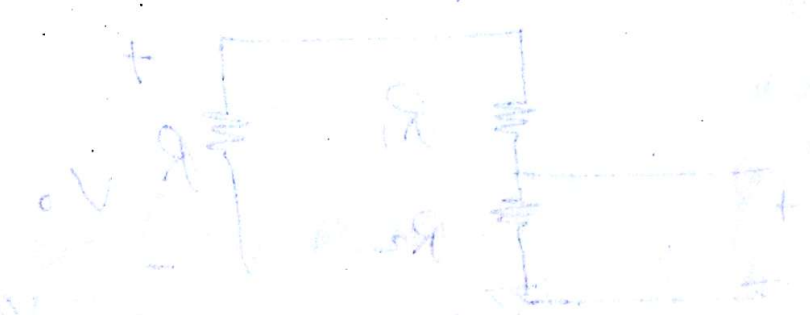$R_{in} = R_{if} - R_s$ $R_{out} = \frac{1}{\frac{1}{R_{of}} - \frac{1}{R_L}}$
 series — shunt



$\frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} = \frac{1}{1 + \frac{R_1}{R_2}}$

8

Series - Series F.B

voltage Gain μ $R_{id} = 10k$ $V_o = 10$

find $A_f = \frac{V_o}{V_s}$ & R_{in} & R_{out}



a) $\mu = 10^5$ V/V

$R_1 = 100\Omega$


b) $\mu = 10^4$ V/V

$R_1 = \infty$


Series - Series

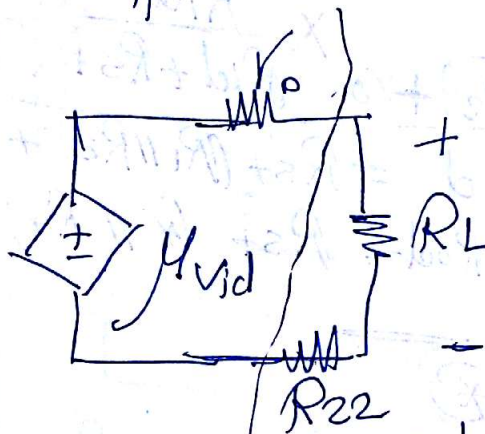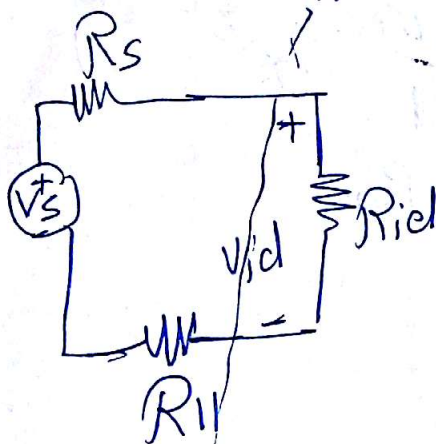

model of opamp

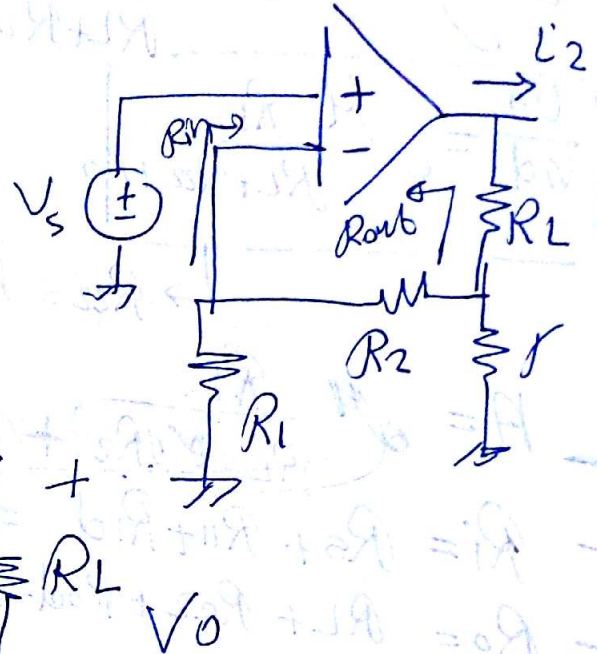

Feedback Analysis

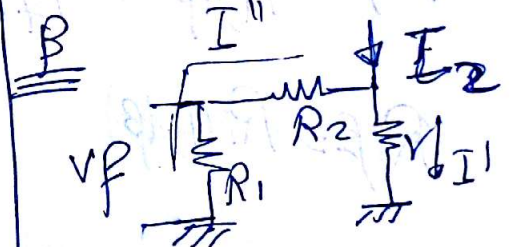


$$V_F = I'' R_1$$

$$I'' = I_2 \times \frac{R_2}{R_1 + R_2}$$

$$V_F = I_2 \times \frac{R_1 R_2}{R_1 + R_2}$$

$$\beta = \frac{V_F}{I_2} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{22} = V_F / I_2$$

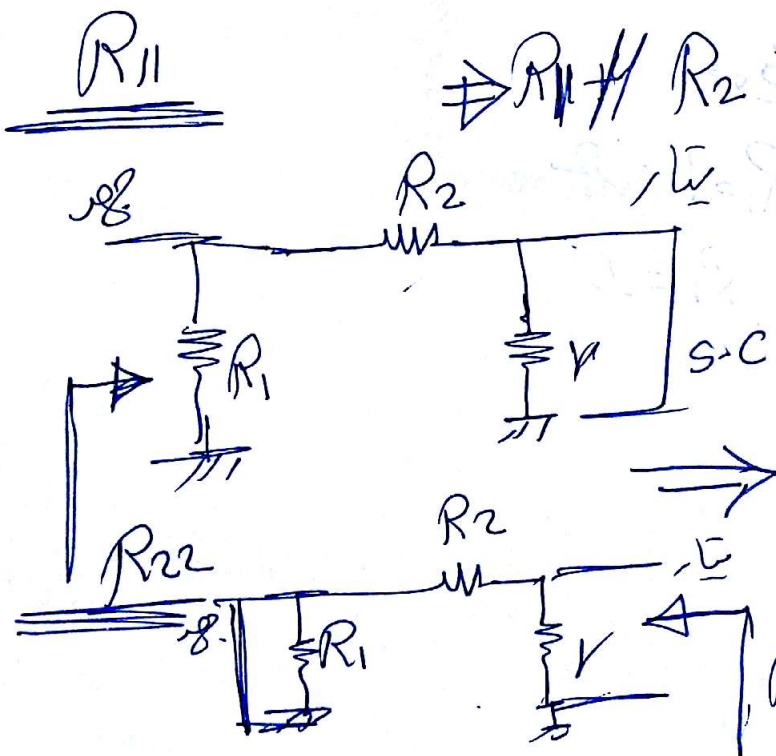

$$A = \frac{V_o}{V_s} = \frac{V_o}{V_{id}} \times \frac{V_{id}}{V_s}$$

(6)

$$V_o = \mu V_{id} \times \frac{R_L}{R_L + R_{22} + r_o}$$

$$\left| \frac{V_o}{V_{id}} = \mu \frac{R_L}{R_L + R_{22} + r_o} \right|$$

$$V_{id} = V_s \frac{R_{id}}{R_{id} + R_s + R_{11}}$$

$$\left| \frac{V_{id}}{V_s} = \frac{R_{id}}{R_{id} + R_s + R_{11}} \right|$$

$$\rightarrow R_{22} = r_o \parallel R_2$$

$$\rightarrow R_{11} = R_1 \parallel R_2$$

$$- A = \mu \frac{R_L}{R_L + (r_o \parallel R_2) + r_o} \times \frac{R_{id}}{R_{id} + R_s + (R_1 \parallel R_2)} \quad (*)$$

$$- R_i = R_s + R_{11} + R_{id} = R_s + (R_1 \parallel R_2) + R_{id}$$

$$- R_o = R_L + R_{22} + R_{od} = R_s + (r_o \parallel R_2) + R_{od}$$

$$A_f = \frac{A}{1 + A\beta} = \frac{(*)}{1 + (*) r R_1}$$

$$R_{if} = R_i (1 + A\beta) \quad R_{of} = R_o (1 + A\beta)$$

عضو

$$a) \mu = 10^5 \quad R_1 = 100 \Omega$$

$$b) \mu = 10^4 \text{ V/V} \quad R_1 = \infty$$

Sheet 2
Electronic Circuits & Measurements
Feedback

8.1.1

- 8.1.1 (1) A -ve FB amplifier has a closed loop gain $A_f = 100$ and an open-loop gain $A = 10^5$. What is the feedback factor β ? If a manufacturing error results in a reduction of A to 10^3 , what closed loop gain results? What is the % change in A_f corresponding to this factor of 100 reduction in A ? (1)

8.5

- (2) For the -ve FB structure, find the loop gain $A\beta$ for which the sensitivity of closed loop gain to open loop gain $[(dA_f/\beta_f)/(dA/A)]$ is -20 dB. For what value of $A\beta$ does the sensitivity become $\frac{1}{2}$?

8.13

- (3) A particular amplifier has a non-linear transfer ch^t that can be approximated as follows.

a) for $|V_I| \leq 10 \text{ mV}$ $V_O/V_I = 10^3$

b) for $10 \text{ mV} \leq |V_I| \leq 50 \text{ mV}$ $V_O/V_I = 10^2$

c) for $|V_I| \geq 50 \text{ mV}$ OP saturates

If the amplifier is connected in a -ve FB loop, find the FB factor β that reduces the factor of 10 change in gain to only a 1% change. What is the transfer ch^t of the amplifier with FB?


Ans

- (4) A series-shunt draws the series-shunt FB amplifier. Using


8.14 $V_s = 100 \text{ mV}$, $V_f = 90 \text{ mV}$ and $V_o = 10 \text{ V}$. What are the corresponding values of A and β ?

8-9

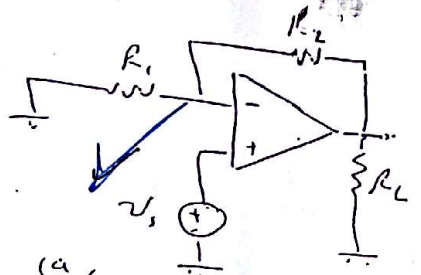
- (15) For each of the following op-amp circuits, identify the feedback topology and indicate the output variable being sampled and the feedback signal. Find expression for β and hence find A_f .




(a) series-shunt

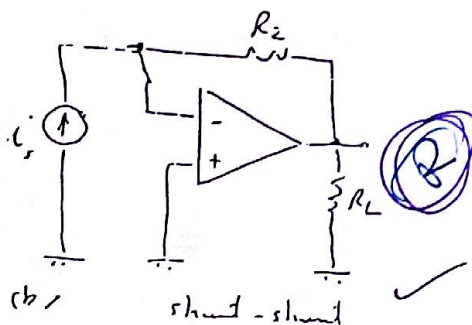

(b) shunt-shunt

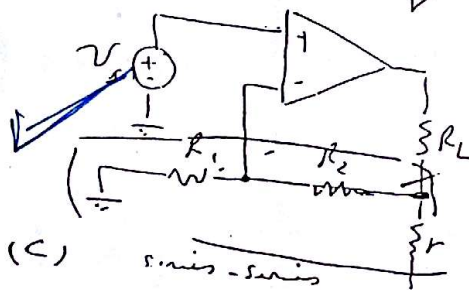

(c) series-series

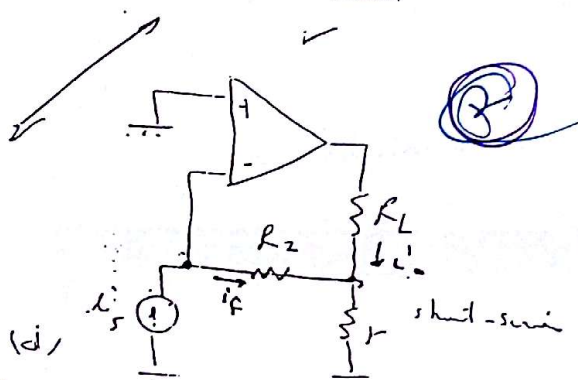


(d) shunt-series

8-20

- (6) A series-shunt FB amplifier employs a basic amplifier with input and output resistances each of $1\text{ k}\Omega$ and gain $A = 2000\text{ V/V}$. The FB factor $\beta = 0.1\text{ V/V}$. Find the gain, A_f , and i_{ip} and i_{op} resistances R_{if} , R_{of} .

- (7) A series-series FB amplifier employs a transconductance amplifier having $G_m = 100\text{ mA/V}$; i_{ip} resistance of $10\text{ k}\Omega$, and i_{op} resistance of $10\text{ k}\Omega$. The FB network has $\beta = 0.1\text{ V/A}$, an i_{ip} resistance (with port 2 open-circuited) of $10\text{ k}\Omega$, and an i_{op} resistance (with port 2 open-circuited) of $10\text{ k}\Omega$. The amplifier operates with a signal source having $R_{sig} = 10\text{ k}\Omega$, and with $R_L = 10\text{ k}\Omega$. Find A_f , R_{in} , R_{out} .

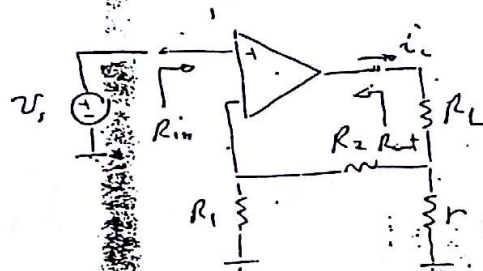Q.80 For the series-series FB amplifier shown, the op-amp is characterized by an open-loop voltage gain μ , $R_{id} = 10 \text{ k}\Omega$, $r_o = 100 \Omega$, $R_L = 1 \text{ k}\Omega$. The FB network has $R_1, R_2 = 10 \text{ k}\Omega$, and $r = 100 \Omega$. Find $A_f = i_o / v_s$, R_{in} , R_{out} for: a) $\mu = 10^5 \text{ V/V}$, $R_1 = 10 \text{ k}\Omega$ b) $\mu = 10^4 \text{ V/V}$, $R_1 = 10 \text{ k}\Omega$




- Q.9 For the amplifier network shown
- Identify the FB connection type
 - Draw the equivalent circuit of the amplifier considering the loading effect of the FB circuit
 - Find expressions, then calculate the numerical values for A , β , A_f , R_{if} , and R_{of} .

given: $R_L = R_D = 10 \text{ k}\Omega$

$g_{m1} = 4 \text{ mA/V}$, $r_o = 100 \text{ k}\Omega$

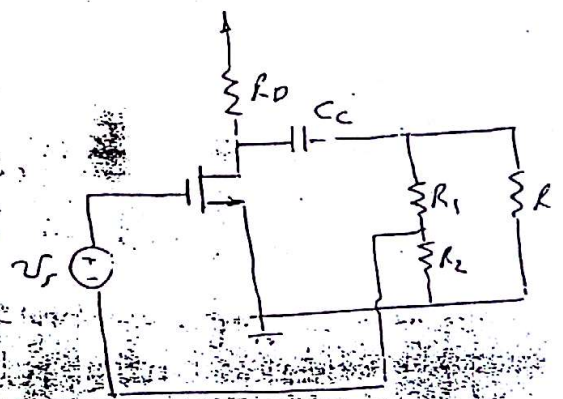$R_1 = 80 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$



*What is feedback

Feedback.

المقصود بالـ feedback هو أخذ جزء من الخرج و يتم ارجاعه مرة أخرى الى الدخل

-ve feedback

اذا تم ارجاعه الى الـ IP موجب ←

+ve feedback

الب ←

-ve F.B
used in
amplifier


&

+ve F.B
used in
oscillators

-ve F.B → feedback signal is out of phase of i.p
phase shift = 180°

+ve F.B → " " " " in phase " "
phase shift = 0°

*The General feedback structure

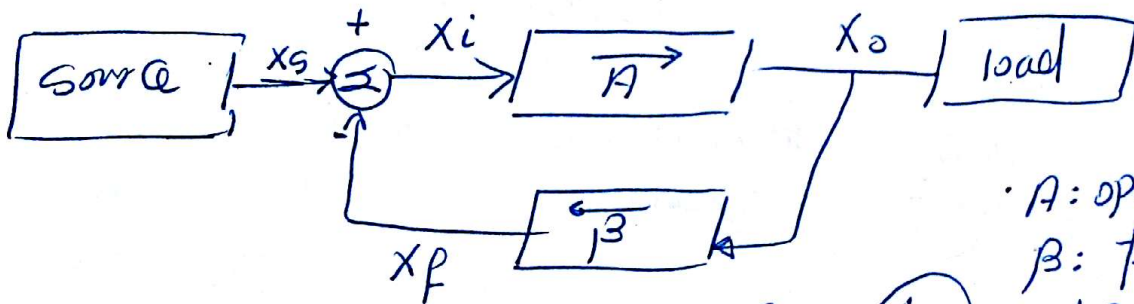

• A: open loop gain
β: feedback parameter
AB: loop gain

$$A_f = \frac{A}{1 + AB} \quad AB \gg 1 \quad \approx \frac{A}{AB} \approx \frac{1}{\beta}$$

* feedback types There are 4 types of feedback

↳ series-shunt

↳ series-series

↳ shunt-shunt

↳ shunt-series



↓

↓

لغودى الـ input

لغودى الـ o.p

Series - Shunt Feed back

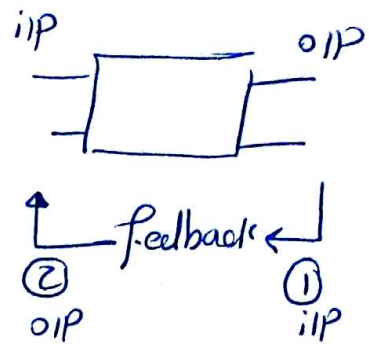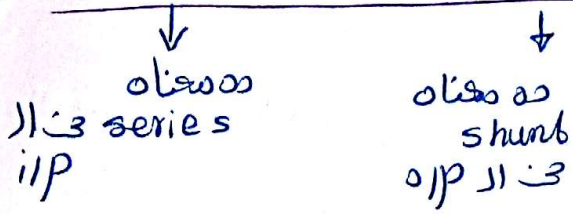

Note


a/p
Current feedback = series \Leftarrow لذلك تسمى

عند (1)
حافظ اعمل feedback لتيار الخرج
توازي ها فذ I_o

voltage feedback = parallel \Leftarrow لذلك تسمى v/p

عند (2)
حافظ اعمل feedback لجهد الخرج
توازي ها فذ V_o
عاوز ادخل ال feedback على اذن

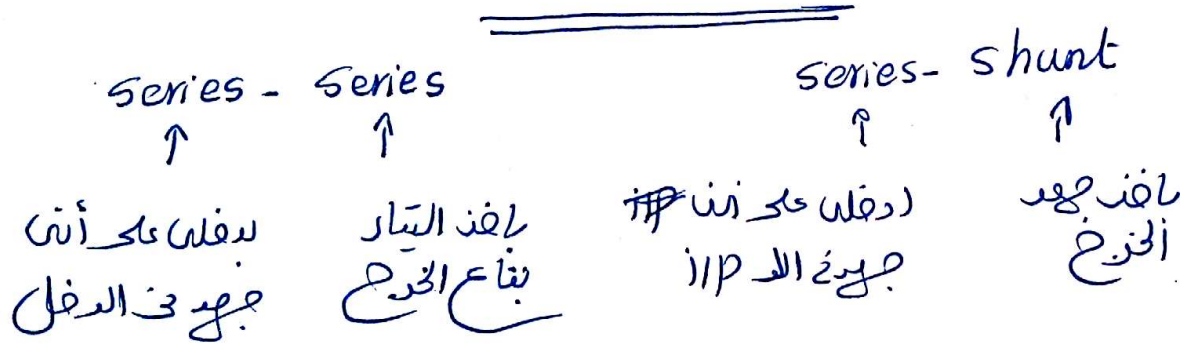Called shunt \Leftarrow لتيار في الدخول
Called series \Leftarrow لجهد في الدخول



في المعاضه
analysis
افيد
model
+ R_{11} R_{22}
 R_i , R_o , A_v , β

[1] -ve F-B, $A = 10^5$ "open loop gain" $A_f = 100$ Find feedback factor β ??

manu factoring error in $A \rightarrow A_{new} = 10^3$

what is the closed loop gain

what is the % change in A_f

$$A_f = \frac{A}{1+A\beta} \rightarrow A\beta = \frac{A}{A_f} - 1 = \frac{10^5}{100} - 1 = 999$$

$$\beta = \frac{999}{10^5} = 9.99 \times 10^{-3} \#$$

$$\text{at } A = 10^3 \rightarrow A_f = \frac{A}{1+A\beta} = \frac{10^3}{1 + 10^3 \times (9.99 \times 10^{-3})}$$

$$A_f = 90.99$$

$$\frac{dA_f}{A_f} = \frac{A_{f_{new}} - A_{f_{old}}}{A_{f_{old}}} = \frac{90.99 - 100}{100} \times 100 = -9\% \#$$

[2] -ve F-B, Find Loop Gain $A\beta$, sensitivity of $\frac{\text{Closed loop gain}}{\text{open loop gain}} = -20 \text{ dB}$
For what value of $A\beta$ does the sensitivity become $\frac{1}{2}$

$$\frac{dA_f}{A_f} / \frac{dA}{A} = \frac{1}{1+A\beta} = \text{sensitivity} = -20 \text{ dB}$$

$$= 1+A\beta = 20 \text{ dB}$$

$$20 \log(1+A\beta) \Big|_{\text{ratio}} = 20 \text{ dB}$$

$$1+A\beta = 10$$

$$A\beta = 9 \#$$

$$\frac{1}{1+A\beta} = \frac{1}{2}$$

$$1+A\beta = 2$$

$$A\beta = 1 \#$$

amplifier has particular non linear CLC

can be approximated as follows

- for small signal $\rightarrow |V_i| < 10\text{mV} \rightarrow \frac{V_o}{V_i} = 10^3$

- for intermediate input signal $\rightarrow 10\text{mV} \leq |V_i| \leq 50\text{mV} \rightarrow \frac{V_o}{V_i} = 10^2$

for large signal $\rightarrow |V_i| \geq 50\text{mV}$

• The amplifier connected in $-ve$ F.B \rightarrow Final β

feedback factor ??
that reduce the factor of gain to only 10% change (at $V_i = 10\text{mV}$)

• what is the CLC of amplifier with F.B ??

reduce = 10%
remain = 90%

$$A_{F2} = 0.9 A_{F1}$$

$$\frac{100}{1+100\beta} = 0.9 \frac{10^3}{1+10^3\beta} \rightarrow \beta = 0.08$$

$$A_F = \frac{A}{1+A\beta}$$

$$A_{F1} = \frac{10^3}{1+10^3(0.08)} = 12.84 \rightarrow |V_i| \leq 10\text{mV}$$

$$A_{F2} = \frac{10^2}{1+10^2(0.08)} = 10.1 \rightarrow 10\text{mV} \leq |V_i| \leq 50\text{mV}$$

then o/p saturated $\rightarrow |V_i| \geq 50\text{mV}$

How

$$\frac{V_i}{A=10^3} \rightarrow \frac{V_i}{A=10^2}$$

Feedback

$$\frac{V_i}{A_F=12.4} \rightarrow \frac{V_i}{A_F=10}$$

معدل التغير في A_F اقل من معدل تغير A

5) Series-shunt $\bar{F}-B$

amplifier \rightarrow i/p & o/p resistors = 1K

$$\text{Gain} = A = 2000 \text{ V/V}$$

Feedback parameter $\beta = 0.1 \text{ V/V}$

Find A_f , i/p , o/p R_{if} of R_{of}


op-amp

$$A_f = \frac{A}{1+A\beta} = \frac{2000}{1+2000 \times 0.1} \quad \#$$

$$R_{if} = R_i(1+A\beta) = 1K [1+2000 \times 0.1] \quad \#$$

$$R_{of} = \frac{R_o}{1+A\beta} = \frac{1K}{(1+2000 \times 0.1)} \quad \#$$

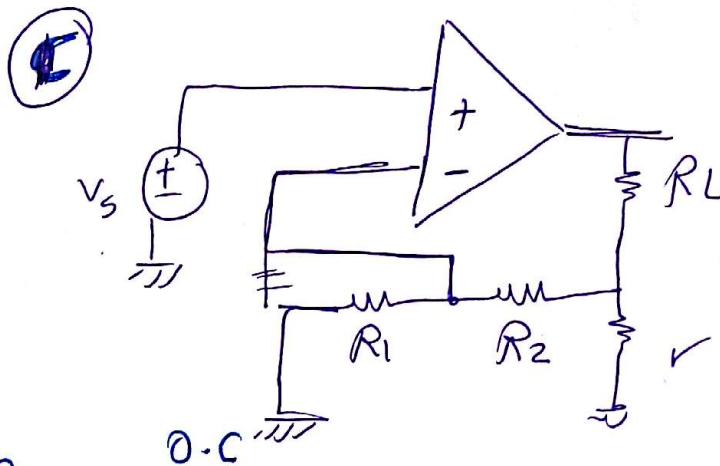5) for each of the following op-amp
 \rightarrow identify feedback topology
 \rightarrow find expression for β and then A_f



$R_L \Rightarrow$ open circuit

$I_f = 0$ \therefore Current feedback

series \leftarrow o/p \therefore series

ویرجیٹ کی ال پ پ ا کی لفظ - : تو


Series-series $\#$

لتیڈ النوع
 \rightarrow put $R_L = o.c$
 if the signal returned
 to the amplifier i/p
 by feedback = 0

\therefore Current feedback
 \rightarrow put $R_L = s.c$

 ----- = 0

\therefore voltage feedback

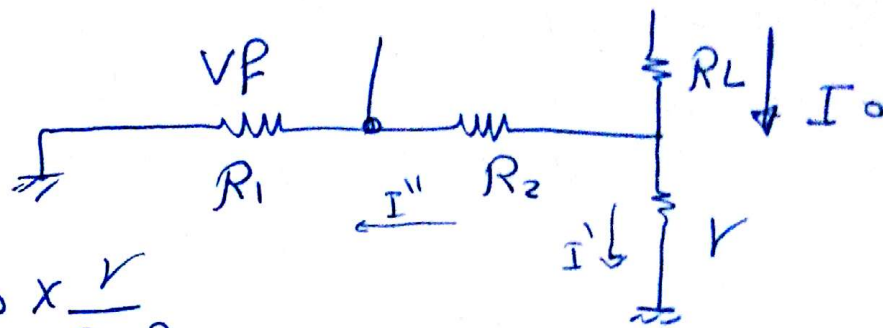


$$I'' = I_0 \times \frac{V}{R_1 + R_2}$$

$$V_F = I'' R_1 = I_0 \frac{V}{R_1 + R_2} R_1$$

$$\beta = \frac{V_F}{I_0} = \frac{V R_1}{R_1 + R_2} \neq$$

$$A_f \approx \frac{1}{\beta} = \neq \frac{R_1 + R_2}{V R_1} = \left[\frac{1}{V} + \frac{R_2}{V R_1} \right] \neq$$

(a)

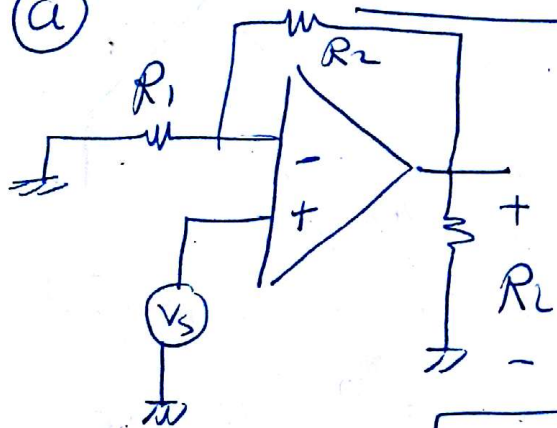

- Put $R_L \Rightarrow S.C$


$$V_F = 0$$

\rightarrow voltage feedback shunt \rightarrow o/p

V_o - voltage across R_1 & R_2

\rightarrow series in i/p

series-shunt

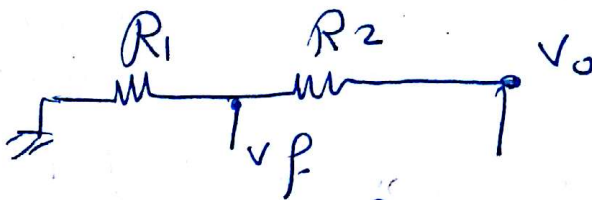

$$V_F = V_o \times \frac{R_1}{R_1 + R_2}$$

$$\frac{V_F}{V_o} = \beta = \frac{R_1}{R_1 + R_2} \neq$$

$$A \approx \frac{1}{\beta} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1} \neq$$